



Topic _____

Date _____



S.No.	Experiment Description	Experiment Date	Submission Date	Remarks Signature
1.	To prepare a job for facing, Turning, Knurling, Tapping, Grooving and Threading as per drawing.	15-04-2021		
2.	To prepare a T-shape and U-shape workpiece by filling, sawing, Drilling, grinding, in fitting shop.	22-04-2021		
3.	To Cast a Component using a single piece pattern in foundry shop.	29-04-2021		
4.	To study the G-M codes for CNC machine and to perform different machining operations including facing, turning, grooving, etc, on CNC lathe	06-05-2021		
5.	To cut a slot on CNC milling machine as per given drawing.	27-05-2021		
6.	To make a hole given diameter on CNC drilling machine.	3-06-2021		

S.No.	Experiment Description	Experiment Date	Submission Date	Remarks / Signature
7.	To study the Construction and working of FDM 3D printing machine.	17-06-2021		
8.	To study construction and working of SLA 3D printing machine.	24-06-2021		
9.	To study the development of drawing using 3D scanner.	01-07-2021		
10.	To study Plastic processing with injection moulding method.	08-08-2021		

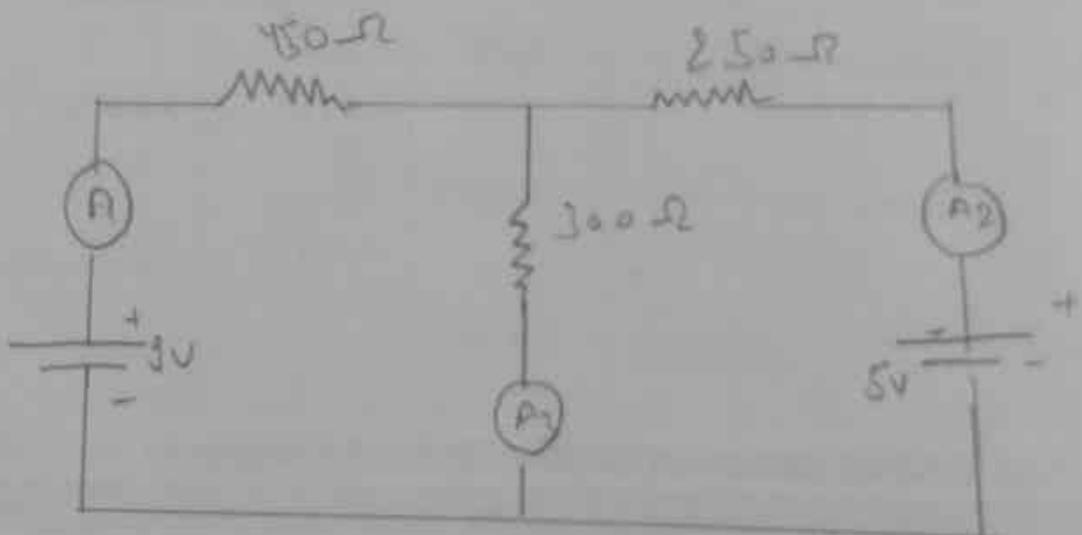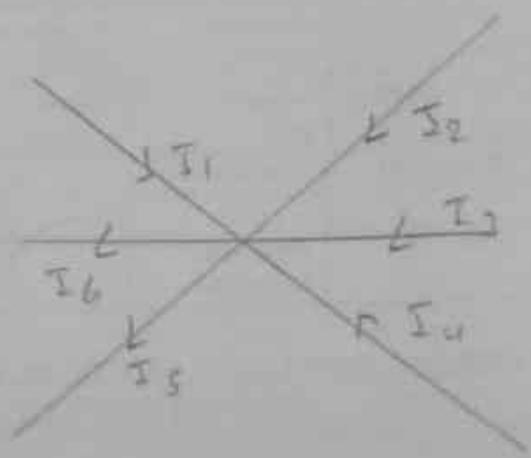

Experiment No: 1

Objective:- Verification of Kirchhoff's Law.

Apparatus required:

No.	Apparatus	Type	Specification/Range	Qty
-	Experimental Board			1
	Power Supply	DC	9V 15V	1
	Voltmeter	DC	0-15V	1
-	Ammeter	DC	0-100mA	1

Connecting wires.

Theory :

- Kirchhoff's Current Law :

In state that the total algebraic sum of current net meeting at the junction is zero. This law is based on the principle of conservation of charges.

KCL at junction "O"

$$I_1 + I_2 + I_3 + I_4 - I_5 - I_6 = 0$$

S.No.	I_1 (mA) Practically	I_2 (mA) Practically	I_3 (mA) Practically	I_3 (mA) Calculated	$I_3 = I_2 + I_1$
L-	10 mA	3 mA	13 mA	13.65 mA	13 mA.

$$450I_1 + 300I_3 = 9 \quad \textcircled{1}$$

$$250I_1 - 550I_3 = -5 \quad \textcircled{2}$$

$$I_1 = 10.6 \text{ mA} \quad \text{Ans}$$

$$I_2 = -3.125 \text{ mA}$$

$$I_3 = 13.65 \text{ mA}$$

$$\text{i.e. } I_1 + I_2 + I_3 + I_4 = I_5 + I_6$$

Procedure :-

- Connect the circuit as shown in circuit diagram.
- Switch on the power supply.
- Note the reading of ammeters.

Calculation of current I_3

$$I_3 = I_2 + I_1$$

Precautions :-


- All the connections should be tight.
- Before connecting the instruments check their zero reading.
- The terminal of resistance should be properly connected.

Result :-

Add the reading of Ammeter 1 (A_1) and Ammeter 2 (A_2) and it will be equal to reading of ammeter 3 (A_3).

$$I_3 = I_2 + I_1$$

NCL is verified.

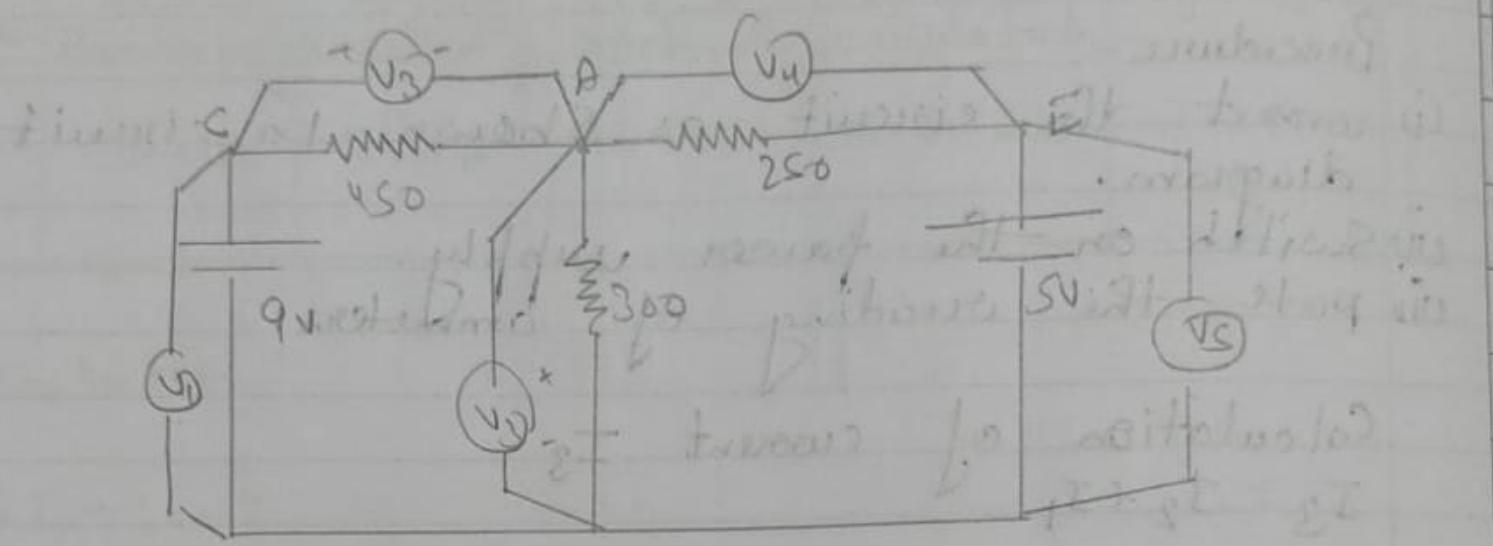

• Zij het de bladde eruit voordat ik dit
 druk tekenen kan ik het niet meer uitleggen
 of de bladde eruitvoer ik dat moet ik
 het nu wel uitleggen

• In de volgende tekening zijn de
 bronnen en de weerstanden in de
 richting van de polairen van de
 bronnen geplaatst

• De rest is gelijk

• De rest is gelijk

Kirchhoff's Voltage Law :-

It States that - the algebraic sum of voltages through a closed loop is zero. This law is based on the principle of conservation of energy.

$$\sum_{i=1}^k V_i = 0$$

$$\sum_{i=1}^k V_i + \sum I R = 0$$

Procedure :-

- Connect the circuit as shown in the circuit diagram.
- Switch on the power supply.
- Note the reading of voltmeters V_1, V_2, V_3, V_4, V_5 (with both polarity).

Precautions :-

- All connections should be tight.
- Before connecting the instruments check their zero reading.
- The terminals of resistance should be properly connected.

S.No.	V_1 (volt) Practically	V_2 (volt) Practically	V_3 (volt) Practically	$V_3 + V_2 - V_1$
1.	9V	-4.8V	-4.2V	$-4.2 - 4.8 + 9 = 0$
2.	V_3 (volt) -4.1V	V_4 (volt) -0.8	V_5 (volt) 8V	$V_3 + V_4 - V_5 = -0.1$

Exp No.

Date / /
Page No.
Shivalal

Result :-

The algebraic sum of v_1, v_2, v_3 equals to zero
 $v_3 + v_2 + v_1 = 0$ for loop 1.


The algebraic sum of v_3, v_4, v_5 equals to
zero $v_3 + v_4 + v_5 = 0$ for loop 2.

KVL is Verified.

Teacher's Signature

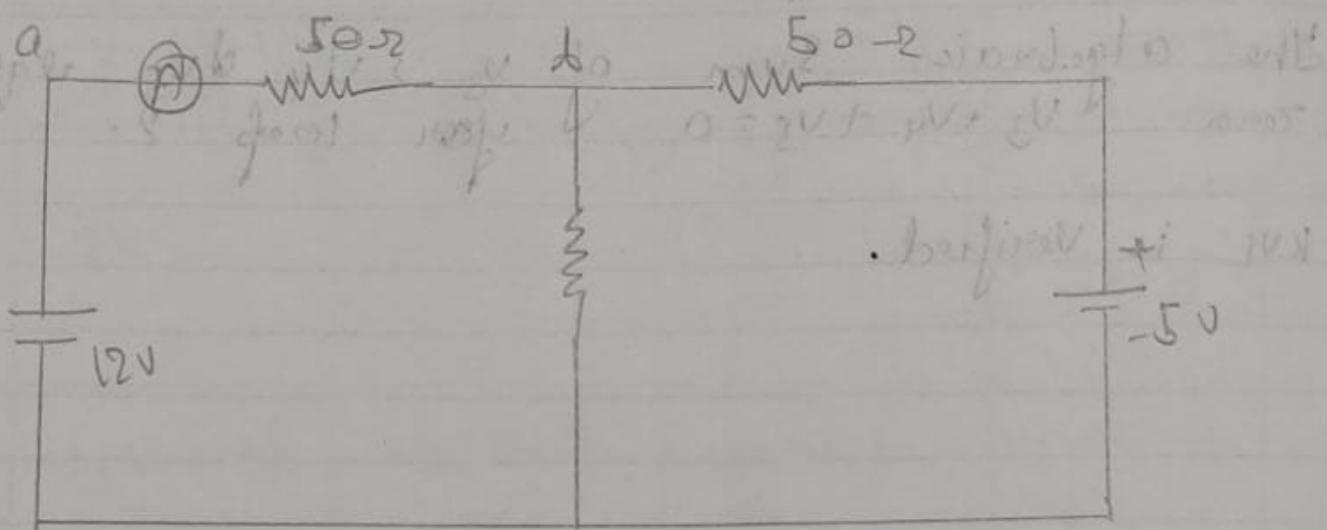- 112.9

at stamp given to me readings at
100% ref. point out by



Exp No. 2

Date / /
Page No.
Shivalal

Experiment No. 2

Objective :- Verification of Superposition theorem.



Apparatus required:

S.No.	Instruments	Type	Range/Specification	Qty.
1-	Supply	DC	0-12V	1
2-	Experimental board			1
3-	Voltmeter	MC	0-15V	1
4-	Ammeter	MC	0-10mA	1
5-	Resistance	CPR/MFR	.50Ω	2
6-	Resistance	CFR/MFR	50Ω	1
7-	Connecting leads.			As required

Theory :-

This theorem states that in a linear bilateral network containing several sources the overall response at any point in the network equal the sum of the responses of each individual sources considered.

Teacher's Signature

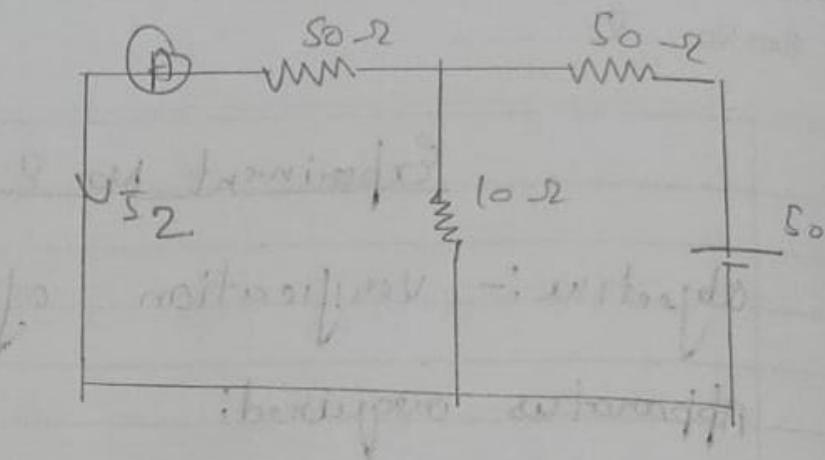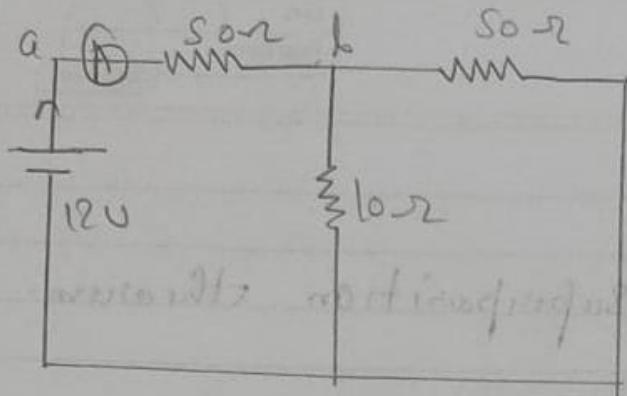

B6 11/03/2010 page 1 of 6 2nd year test 04/2

SNo	Current 'I' (mA) practically C.R.t diagram	Current I_1 (mA) Direct	Current I_2 (mA) practically (C.R.t diagram)	$I = I_1 + I_2$
1	170 mA	180 mA	-10 mA	180 - 10 = 170 mA

calculations:

$$60I_1 - 10I_2 = 12 \quad (i) \quad \text{and} \quad 60I_2 + 5 = 12 \quad (ii)$$

$$T_1 = 0.190 \text{ A} = 190 \text{ mA} \quad T_2 = 1 \text{ mA}$$

$$60I_1' - 10I_2' = 12 \quad (i) \quad I_1' = 0.190 \text{ A}$$

$$I_1' = 0.190 \text{ A} \quad I_2' = -14 \text{ mA}$$

$$\text{current } I_1' = 205 \text{ mA}$$

$$I_1 = I_1' + I_2'$$

current $I_1 = 0.190 \text{ A} + (-14 \text{ mA}) = 0.190 \text{ A} - 0.014 \text{ A} = 0.176 \text{ A}$

$$190 \text{ mA} = 205 \text{ mA} - 14 \text{ mA}$$

current $I_1 = 205 \text{ mA} - 14 \text{ mA} = 191 \text{ mA}$

Exp No.

Date / /

Page No.

Shivalal

Separately with all other sources made
Inoperative one replaced by resistances equal
to their internal resistance.

Procedure :-

Short circuit the terminals

Connect the 12V supply with terminal

Connect the ammeter in series with branch.

Observe the reading of ammeter " I_1 ".

Again short circuit the terminals having

an ammeter in series.

Connect 5V supply with terminal

Observe the reading of ammeter " I_2 ".

Precaution :-

Do not make interconnection on the board
with mains switched ON.


As soon as mains is ON the reading in
the meters must be zero. If the reading in
the meter is not zero check the meter.

Result :-

The net current I is the algebraic sum of
 I_1 & I_2 due to individual voltage source
taking one at a time $I = I_1 + I_2$

Teacher's Signature

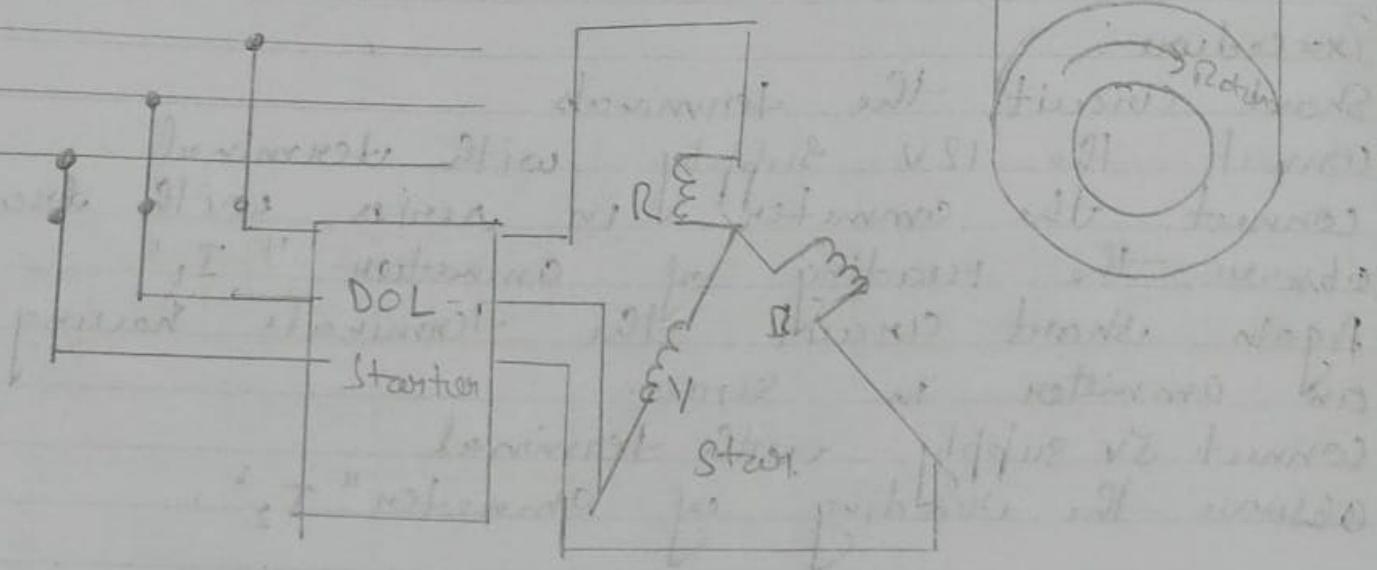Three phase motor starts on full voltage
through starters and therefore no starting
currents, no torque instant start



Circuit diagram for running of induction motor.

Three phase motor starts on full voltage
through starters and therefore no starting
currents, no torque instant start

Three phase motor starts on full voltage
through starters and therefore no starting
currents, no torque instant start

Experiment - 3

Objective :- To Study the running and speed reversal of a three-phase induction motor and record speed in both direction.

Apparatus used :-

S.No	Equipment	Type	Signification	Qty.
1	3-phase induction motor.	Squirrel cage	3-phase, 415v 1440 rpm.	1
2	DOL starter	x		1
3	Tachometer.	Digital	(0-10000) rpm.	1




Theory :-

Three phase Induction motor:-

A machine that converts 3-phase a.c. electrical power into mechanical power by using an electromagnetic induction phenomenon is called as three phase induction motor.

The 3-phase IM are usually built in small size. They are most common used a.c. motor used in industry because they have simple & rugged construction, low cost, high efficiency, reasonably good power factor, self-starting and

Teacher's Signature

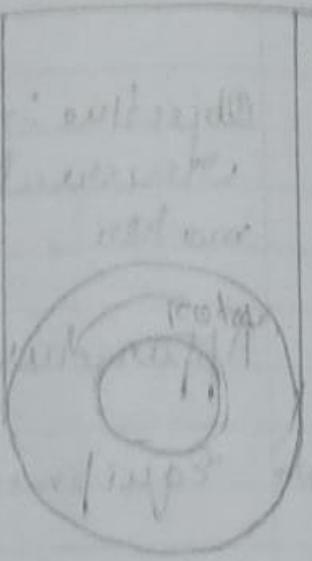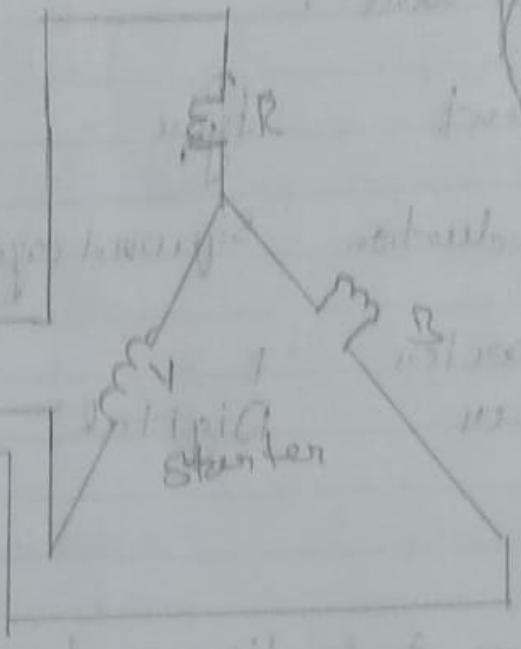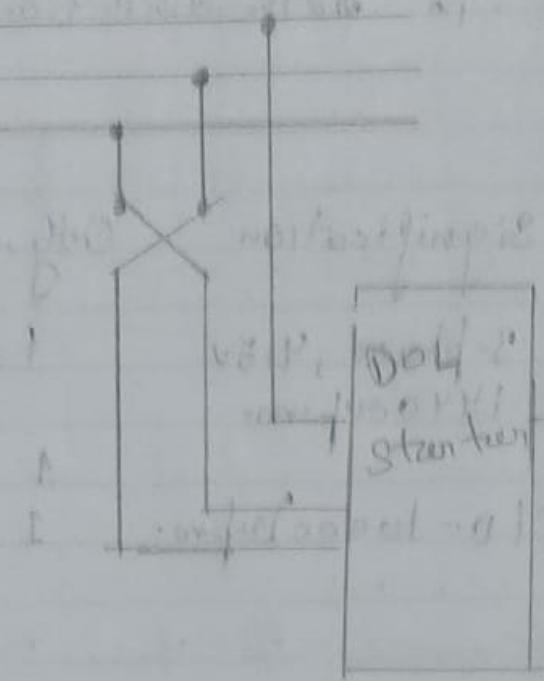

Circuit Diagram for Reviewing the Direction of Rotation of an Induction Motor.

Exp No.

Date / /

Page No.

Shivalal

low maintenance. Almost 90% of mechanical power used in industry is provided by 3-phase induction motor.

Working Principle:-

At starting stationary rotor conductor cuts across the revolving magnetic field produced by the stator. An e.m.f. is induced in them by electromagnetic induction phenomenon. Current flows through the rotor conductors as they are short circuited and produce rotor field. By the interaction of motor and stator magnetic field torque develops in rotor start rotating in the direction of applied field.

Type of Induction Motor:

According to the construction of the motor, there are two types of induction motors namely:

Squirrel cage induction motor.

Slip ring or wound rotor type induction motor.

Starter:

A device used to limit the inrush flow of current at start is known as starter. In this experiment we are going to use

Teacher's Signature

Standard for test because equivalent with
of balance for primary coil test although
not able to reduce voltage to 1000

S.No.	Voltage (V)	Current (Amp)	R.P.M.	Speed by P.T.O.
1.	400 V	9.30	1541	870 - 300 rpm
2.	400 V	7.44	1521	870 - 300 rpm Clockwise

15 x 10 Imp. Output 4.15 A. 3.6 A. 1.4 A. 0.4 A.
and so on. In which the current
will reduce to neglect except last
half bridge if we take the average.

Current will reduced to neglect
and so on. In which the current
will reduce to neglect except last
half bridge if we take the average
of all the current values.

for example first we take all the current
for 15 x 10 Imp. output at half bridge
and so on. Then we take average of all

Exp No.

Date / /
Page No.
Shivalal

In this experiment we are going to use "Direct On Line starters" to start the three phase IM.




Starting of Three-Phase Induction Motors:
At starting 3 phase induction motor takes 5-7 times of full load current & starting torque being $\sqrt{3}$ to 2.5 times of full load torque. Due to this high current the winding of motor & instruments may burn. A Starter is used to keep current within reasonable limits of three phase induction motor, otherwise large starting current may cause undesirable voltage dip in the supply.

Direct on line starters:

A DOL starter essentially consists of a contactor having four normally open (N.O) contacts and a contactor coil also known as no-volt coil. There are two push buttons ON and OFF which are used to start and stop the motor. To protect motor against over load, thermal or magnetic over load coils are connected in each phase.

To start the motor, the ON push button is pressed which energizes the no-volt coil which pulls it plunger up such a direction

Teacher's Signature

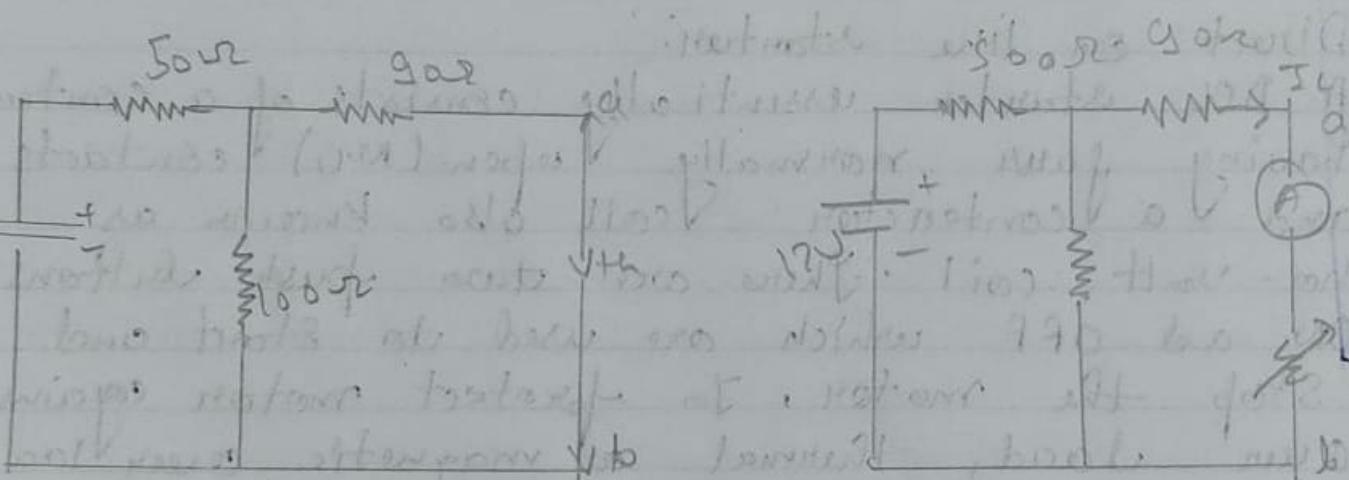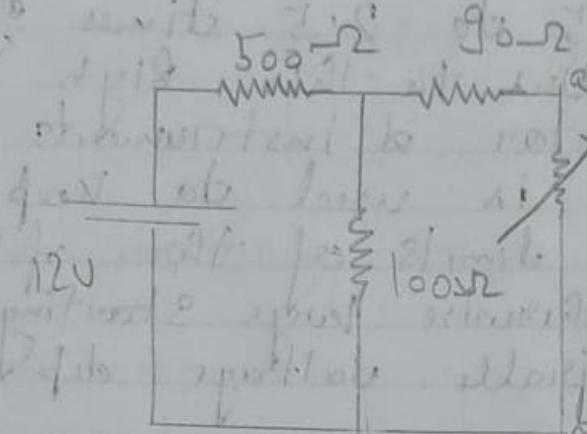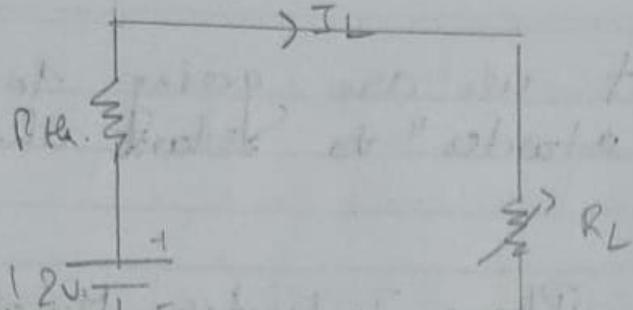

What do we observe? We also attach a step up, return at front of 12v and with a capacitor across the load. In this case, the output is 12v.

that all the normally open (N.O.) contacts are closed and the motor is connected across supply through three contact which keeps the no-volt coil circuit even after the ON push button is released. To stop the motor, OFF push button is pressed momentarily which de-energizes the no-volt coil opening the main contacts.

When the motor is over loaded, the thermal overload relay contact, connected in control circuit opens thus disconnecting the no-volt relay from the supply. Overload protection is achieved by thermal element overload relay. This starter is used only for under 5 H.P. motor.

Reversal of direction of rotation of induction motor:

The direction of rotation of induction motor can be changed by changing the phase sequence of the supply to the stator as by changing the phase sequence, torque is reversed due to reversal of phase sequence rotating in opposite direction. The phase sequence can be changed by interchanging any two supply wires i.e. R-Y-B is changed to R-B-Y.

to R-B-Y.

Procedure :

- (i) Connect the circuit as shown in the circuit diagram.
- (ii) First we put the starter to start position when it gains approx 80% of their rated speed throw it to the run position.
- (iii) Load the machine by tightening the belt till this rated current starts flowing.
- (iv) Interchange the connection of any two phases & then repeat the above procedure.

Precautions :-

- (i) All the connections should be tight.
- (ii) Never touch the live terminal during experiment.
- (iii) Before changing the connection, switch off Supply properly.
- (iv) Insure the load carefully.
- (v) Always use the starter of proper rating.
- (vi) Always wear shoes when working in lab.
- (vii) Make proper contact when measuring the speed with Tachometers.

Exp No.

Date / /
Page No.
Shivalal

Results:


- (i) The induction Motor starting using DOL starter is carried out.
- (ii) It also found that when any two of the phases of three phase supply is interchanged, then the direction of rotation is reversed but magnitude remains the same.

Teacher's Signature

SNO	V _A R - Pract.	V _A through	Prac. Computation	R _L	I _L measured	$\frac{I_L}{V_A} = \frac{V_A}{R_L + R_L}$
1.	8V	2V	173.3	25Ω	0.032A	0.032A
2.	2V	2V	173.3	50Ω	0.04A	0.04A
3.	2V	2V	173.3	100Ω	0.02A	0.02A

Calculation
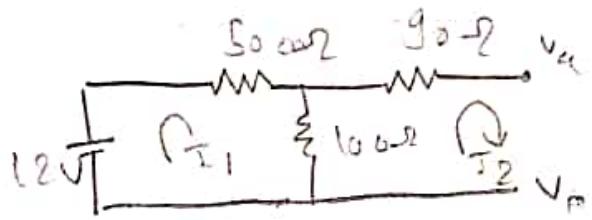
$$R_{th} = \frac{500 \times 100}{600} = 173.3\Omega$$



$$V_a - 50 \cdot I_2 - 100(I_2 - I_1) = V_B$$

$$\Rightarrow V_{th} = V_a - V_B = 2V$$

$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{2}{173.3 + 25} = 0.008A$$

$$\text{When } R_L = 50\Omega$$

$$I = \frac{2}{173.3 + 50} = 0.008A$$

$$\text{When } R_L = 100\Omega$$

$$I = \frac{2}{173.3 + 100} = \frac{2}{273.3} = 0.0073A$$

Experiment No - 4

Objective:- Verification of Thevenin's Theorem.

Apparatus Required:

SNO-	Instrument	Type	Range	Qty
	Supply	DC	0-12V	1
	Experimental board			1
	Voltmeter	MC	0-15V	1
	Ammeter	MC	0-10mA	1
	Resistance	CFR/MFR	50-2	2
	Resistance	CFR/MFR	10-2	1
	Connecting leads			As required.

Theory:

This theory provides a mathematical technique for replacing a two-terminal network by voltage source and resistance R_{th} . According to the Thevenin's theorem "Any linear network containing energy source and resistance can be replaced by an equivalent circuit consisting of voltage source V_{th} in series with R_{th} ". The value of V_{th} is the open circuit voltage between the terminals of network and R_{th} is its resistance measured as short circuit while current

Source treated as open ckt.

Current across load resistance (R_L) is given by Eqn. $I_L = V_{th} / R_{th} + R_L$

Where, V_{th} = open ckt voltage across the terminals.

R_{th} = Eqn. resistance across terminals

R_L = load resistance.

Procedure:-

- Connect the ckt according to fig (a); observe V_{AB} .
- Connect the ckt according to fig (b); observe I_1


Precautions:-

Do not make interconnection in board with main switch ON.

As soon as mains is ON, the reading in meter must be zero. If the reading is not zero, chuck the meter again.

We find that calculated value of load current " I_1 " is equal to measured " I_1 ".
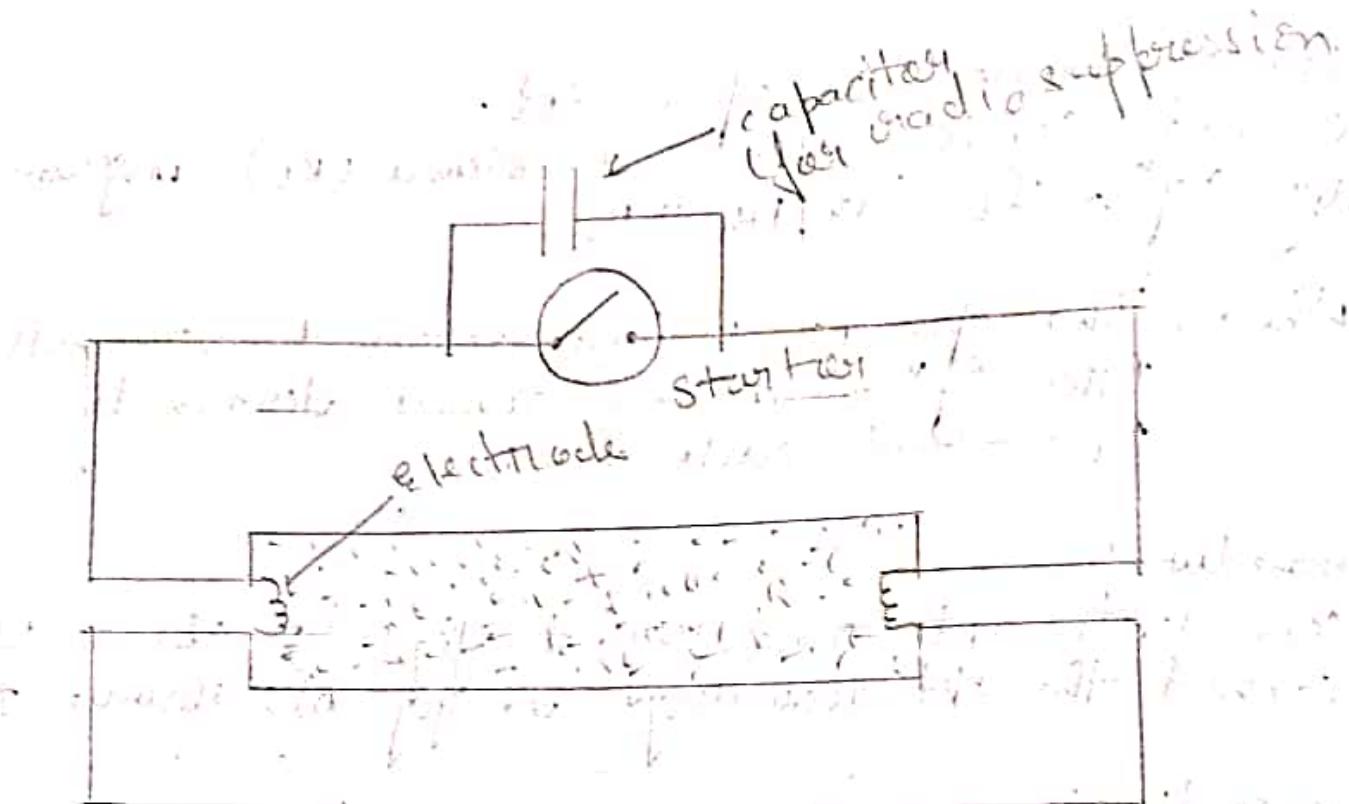
$$I_1(\text{calculated}) = I_1(\text{measured}).$$



FLUORESCENT LAMP CIRCUIT

electrodes is required for ionisation of gas and is caused by combined action of choke coil and starter. The arrangement of fluorescent lamp circuit is shown in the fig.

When fluorescent lamp is switched on the starter makes and breaks the circuit rapidly resulting in high rate of change of current through choke and starter. The voltage across the choke is given as


$$v = L \frac{di}{dt}$$

high rate of a change of

current through coil causes high voltage across choke and gas discharge starts. The resistance of ionized gas decreases rapidly due to it has negative resistance characteristics. The lamp tends to draw very dangerous high current, but prevented by choke coil.

Result:

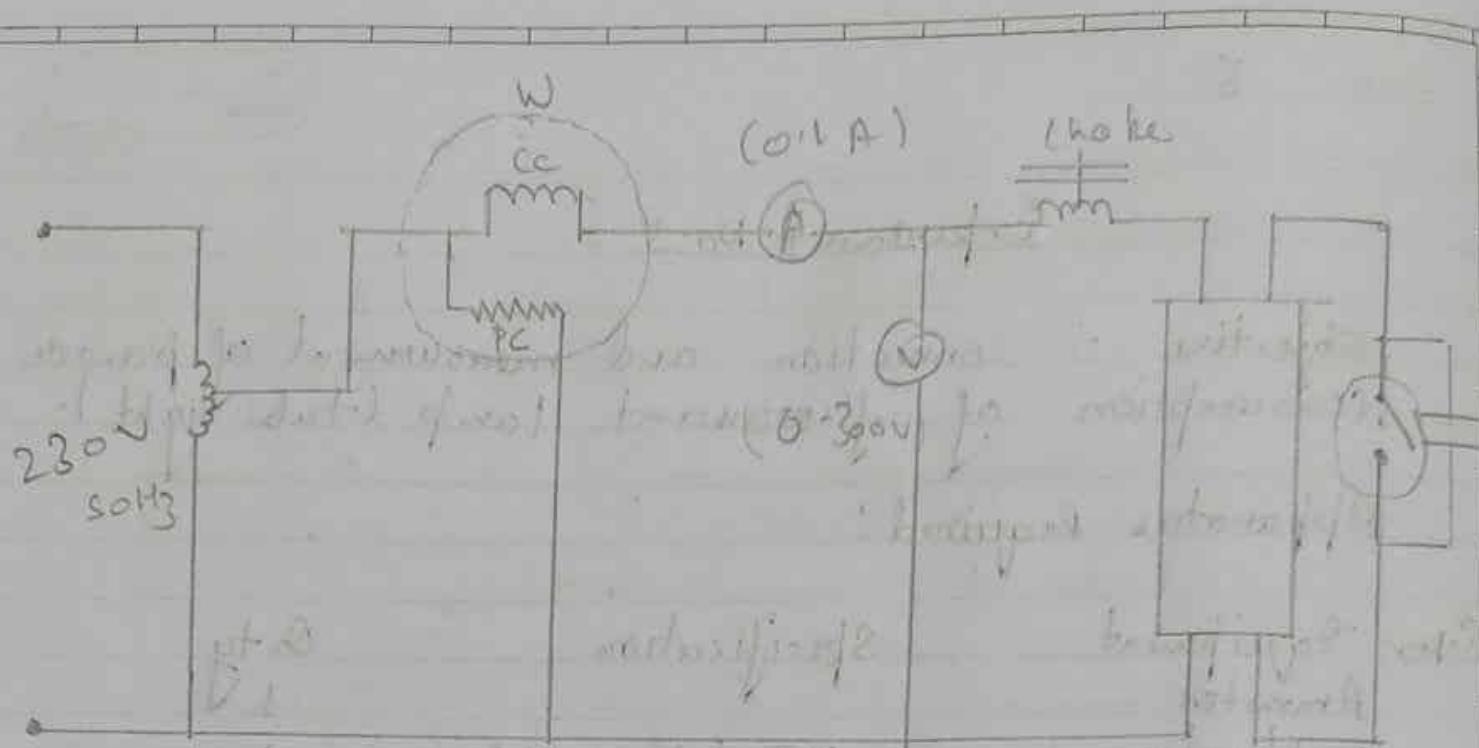The working and operation of F.L is studied. Power factor of FL is also measured, the choke coil in series with FL have very low power factor which is undesirable.



Circuit diagram for determine of Power factor of fluorescent lamps.

$$\text{Power factor} = \cos \phi = \frac{P}{VI} = \frac{W}{VI}$$

Voltage across AC source (LLV)	Current Draw By FL (I)	Power consumed (W)	$\text{P.F.} = \frac{W}{VI}$
220V	0.66 A	80W	$\frac{80}{220 \times 0.66} = 0.24$

Experiment - 6

Objective :- Measurement of Power and power factor in a single phase AC series inductive circuit and Study improvement of power factor using capacitor.

Apparatus required:

S.No	Equipment	Specification	Qty
1-	Ammeter	MI type, 0-1A	1
	Voltmeter	MI type, 0-250V	1
	Wattmeter	50w, 0-250V, 1A	1
	Fluorescent lamp. with starter & choke coil.	40w, 230V, 50Hz	1
	Auto transformer	1-ph, 30V, 8A	1
	Capacitor	0.5μF, 2.5μF, 3.5μF each 500V	1

Theory :- The fluorescent lamp(FL) is commonly used in houses for lighting. It is discharge lamp in form of tube 35cm in diameter and 0.5m to 1.5m long with an electrode at each end which are in form of coiled filaments coated with electron emitting material. The inside of tube is coated with fluorescent powder as operating temp.

Teacher's Signature.....

John F. G. M. 1903

Pf without c w/vVA (switch open)	Value of c	Pf with Parallel Capacitor w/VVA (switch closed)
$80 / 220 \times 0.66 = 0.55$ ≈ 0.55	reactance of B	$80 / 220 \times 0.75 = 0.75$


a) tube is connected 50°C , no outer tube is required.

A dielectrically high voltage between electrodes is required for ionization of gas and initial starting. This high voltage is caused by combined action of choke coil and standard. The arrangement of LFL circuit is shown in fig 8 below.

When fluorescent lamp is switched on the standard makes and breaks the circuit rapidly resulting in high rate of change of current flowing in it choke and standard. The voltage across the choke is given as $\omega L di/dt$. High rate of change of current through the load causes high voltage across the choke and gas discharge starts. The resistance of ionized gaseous medium rapidly drops due to gas migration resistance characteristics. The lamp itself becomes dangerously high current, but prevented by the inductor coil. The choke coil is in series with fluorescent lamp. Due to low value of inductor factor.

Result :- Power factor is improved.

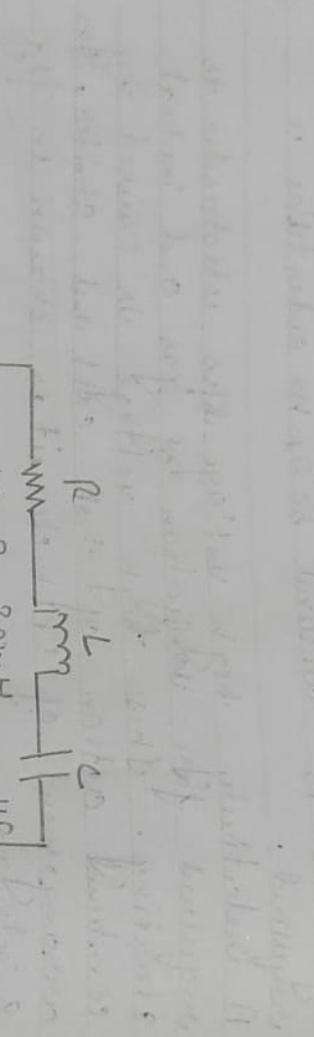W from 0.94 to 0.174 by connecting $C = 10\mu\text{F}$
W from 0.24 to 0.174 by connecting $C = 10\mu\text{F}$



single
oscillator

single stage oscillator
is produced by connecting
the plate load across the output of the oscillator.
The circuit is shown below.
The circuit is called a
single stage oscillator.
The circuit consists of a single
stage of amplification followed
by a single stage of oscillation.
The circuit is shown below.
The circuit consists of a single
stage of amplification followed
by a single stage of oscillation.

single stage oscillator
is produced by connecting
the plate load across the output of the oscillator.
The circuit is shown below.
The circuit consists of a single
stage of amplification followed
by a single stage of oscillation.

S.No	Reading of Signal genera- tor frequency and ratio (V)	Ammeter reading I (mA)	Frequency corresponding to max. current	$f_0 = 1 /$ period
1.	11.15	13		
2.	1.32	15.5	1.92 kHz	1.96 kHz
3.	11.60	18.5		
4.	1.92	20		
5.	12.28	18.5		
6.	12.48	1.7		
7.	12.68	15.6		
8	12.86	14		

2- Percentage error in Resonance frequency

$$\text{error \%} = \frac{f_0(\text{measured}) - f_0(\text{calculated})}{f_0(\text{measured})} \times 100$$

$$= \frac{1.92 - 1.96}{1.92} \times 100$$

$$= \frac{0.04}{1.92} \times 100$$

$$= 0.50\%$$

Experiment No.-7

Objective:- Study the phenomenon of Resonance in RLC series circuit & obtain the Resonance Frequency.

Apparatus:-

SNO.	Equipments	Type	Specification	Qty.
	Single phase AC	AC	230V, 50Hz	1
	Variable frequency signal generator	AC	1Hz - MHz, (0-10)V Sine wave	1
	AC Ammeter	MI	(0-10) mA	1
	Inductors		10, 20, 30 mH	1
	Capacitors		10, 20, 30 nF	1
	Resistors		100 Ω	1
	Connecting wires		PVC insulated	As per requirement

Theory - In a consisting of reactive components of opposite nature i.e. L & C if we change the variable F, L or C there comes a situation when over all impedance (or Admittance) of the circuit becomes purely resistive (or conductive). Such a condition is called "Resonance" of the electric circuit.

electrical circuit.

In resonance condition, output decreases much larger than the excitation.
Let us consider the circuit shown in fig.

Applying KVL we get:

$$\begin{aligned} V &= V_R + V_L + V_C \\ &= IR + j(IX_L - IX_C) \end{aligned}$$

$$\text{where, } Z = R + j(X_L - X_C)$$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2} \quad \text{and the magnitude of current.}$$


$$I = V/Z$$

Now, at resonance we have:

$$\begin{aligned} X_L &= X_C \\ 2\pi f_{resonance} L &= \frac{1}{2\pi f_{resonance} C} \end{aligned}$$

$$\text{Hence, } f_{resonance} = \frac{1}{2\pi \sqrt{LC}}$$

$$\text{Since, } |Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

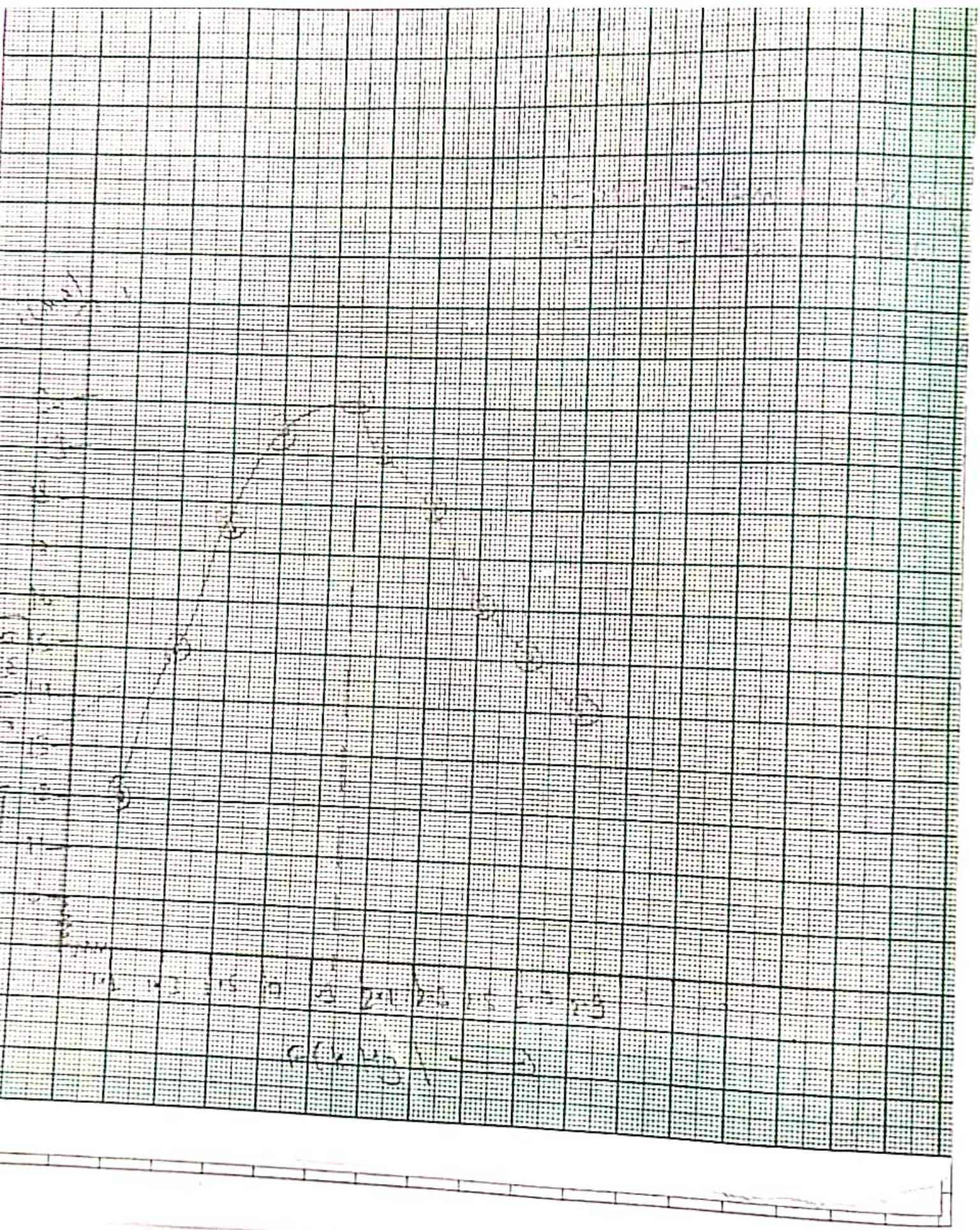

Exp No.

Date	/ /
Page No.	

Shivam

Now, $Z = R$, (as $X_L = X_C$)

$$\therefore I = \frac{V}{R}$$

Variations of current w.r.t. frequency as shown in fig 2. When current is maximum, the circuit is said to be in resonance. So, in resonance condition Z should be minimum. That is, in this condition current is in phase with voltage, power factor become unity & $Z = R$.

Procedure :

Make the connection as per ckt diagram. Switch on the supply keeping switch off of signal generator at initial.

Take the value of frequency at current as per observation table.

Increase the value of frequency & take the readings upto maximum frequency range of available source.

Take atleast 10-12 reading to cover complete range of variations of current around max. value.

Now draw graph between current & frequency.

Teacher's Signature

Exp No.

Date / /
Page No.
Shivalal

Observation:

Value Given : $R = 150 \text{ ohm}$, $L = 3.0 \text{ mH}$,
 $C = 0.22 \text{ nF}$. Applied Voltage $\approx 3 \text{ Volts}$, Frequency
 $\approx 1.96 \text{ kHz}$.

Result :-

Resonance phenomenon is studied successfully and resonance curve is drawn.
The resonant frequency is found to be
 1.96 kHz .

Teacher's Signature

Experiment No.: 8

Objective:- Study and calibration of Single phase energy meters.

Apparatus Required:-

S.No.	Name	Range	Qty
1.	Wattmeter	0 - 750 W	1
2.	Voltmeter	0 - 300 V	1
3.	Ammeter	0 - 10 A	1
4.	Lamp Load bank	1 KW	1
5.	Single phase Energy meter.	600 R/kWh, 50 Hz.	1

Theory:- The total power consumed by load during an interval of time is ENERGY.

$$E = P \times T$$

where E = Energy, P = Power, T = Time.

If the voltage & currents are not constant & have n -values over time t , then.

$$E = \sum_{i=1}^n p_i \cdot t_i \rightarrow \sum_{i=1}^n v_i i_i t_i$$

and it can also be expressed as continuous integral of Power i.e.

Teacher's Signature


$$E = \frac{1}{2} \int_{t_1}^{t_2} P dt = \int_{t_1}^{t_2} VI dt$$

The unit of energy is watt second or joule. But its commercial unit is kilowatt-hour which is defined as energy consumed by load of 1000 W over a period of one hour.

Energy Meter:- Induction type energy meters are most common form of Stein AC kWh meter used to measure the energy consumed in any ac circuit in a prescribed period. When supply voltage & frequency are constant, in day-to-day life in industrial installation. Energy meter is an integrating instrument which measures the total quantity of electrical energy supplied to the circuit in given period.

Principle:- The basic principle of induction type energy meter is electromagnetic induction. When an alternating current flows through two suitably located coils current coil & potential coil) produced rotating magnetic field which is cut by metallic disc suspended near to coils, thus, a current is induced in thin

Power Amplifier

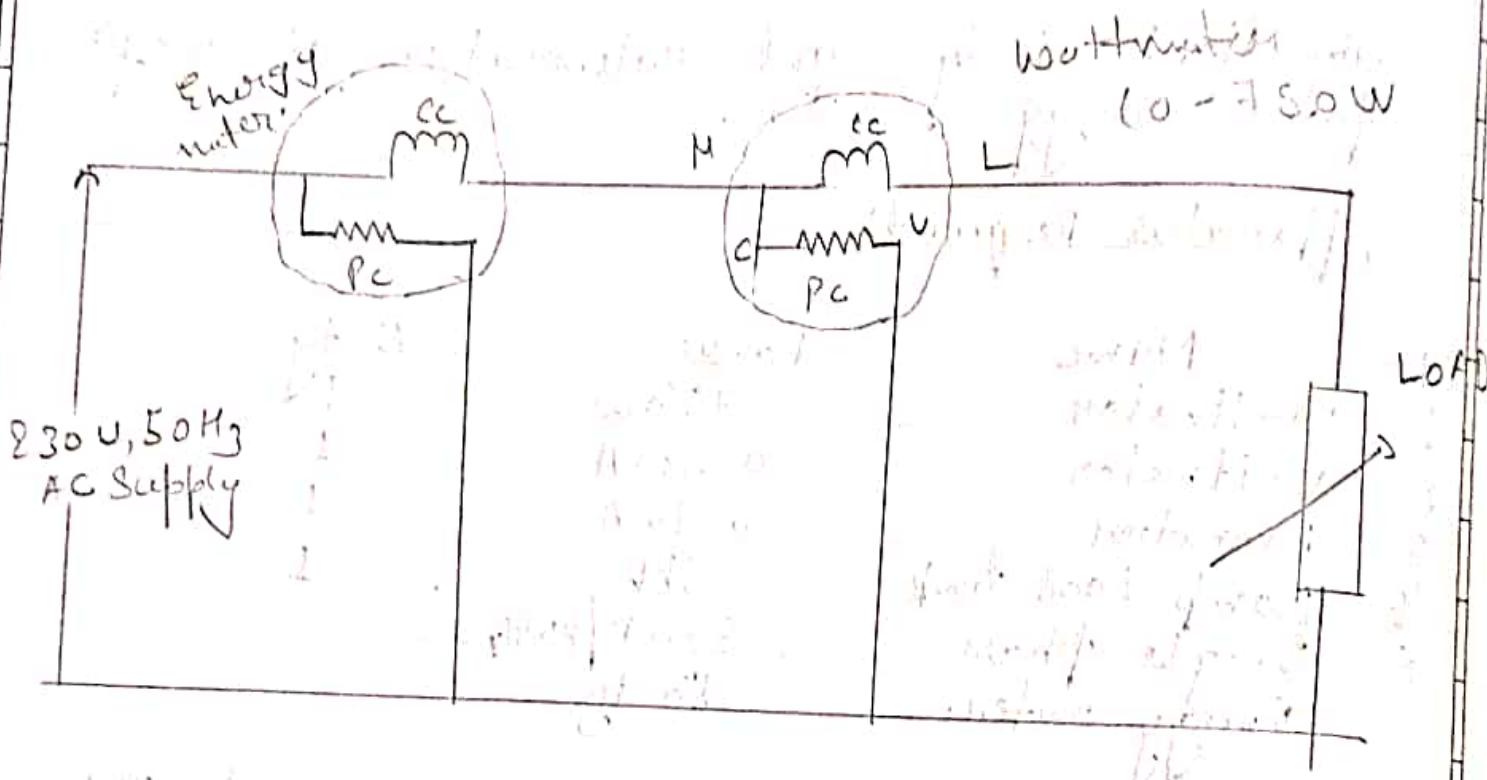

and output stage of which off course
is the load of the stage

and the output stage of which off course
is the load of the stage

$$I_{\text{load}} = \frac{V_{\text{load}}}{R_{\text{load}}} = \frac{100}{100} = 1 \text{ A}$$

and the output stage of which off course
is the load of the stage

1. $E_{st} = \frac{P}{k}$ $E_{st} = \frac{P}{K}$ $E_{st} = \frac{P}{K}$

2. During all breaking times we measured time with
the help of stopwatch and power was measured with
the help of ammeter. We also measured current with
the help of ammeter. $K = 600$ is water constant.

S.No	Power kw	Time (sec)	No. of cavitations	$E_{st} = P/t$	$E_{st} = \frac{kw \cdot t}{3600}$	$\eta_{economics} = \frac{E_{st} - E_{fr} \cdot k \cdot t}{E_{st}}$
1	0.4	32.9	2	0.0033	0.0037	10.81
2	0.6	21.56	2	0.0033	0.0025	5.71
3	0.8	23.62	3	0.005	0.0052	3.84

3. From the above experiment, we can say that
different values of load factor has different
power output and efficiency.

4. We can say that effect of load factor and load factor
has direct relationship. As load factor increases
efficiency decreases and power output
increases. The relationship between load factor
and efficiency is non linear. It is a curve.
As load factor increases efficiency decreases
and power output increases.

Exp No.

Date / /
Page No.
Shivalal

Aluminium disc which circulates eddy current in it.

Construction: An induction type single phase energy meter, has following main parts of operating mechanism:

1) Driving System
2) Braking System

3) Moving System
4) Regulating System

1) Driving System → Develops torque to rotate the moving system. It consists of two electro magnetic coil one is formed by current coil & other one is by voltage coil or pressure coil.

2) Moving System: Essentially consists of aluminium mounted on spindle which is supported by Pivot-jewel Bearing System.

3) Braking System: consist of permanent magnet of C shape covering a part of rotating disc to provide torque.

4) Regulating System → keeps record of energy consumed by load through worm & gear on opinion gear mounted with spindle of moving disc.

Teacher's Signature

Working - When energy meter is connected in circuit, the current coil carries the load current and pressure coil carries the current to supply voltage.

The reading of energy meter is $\Rightarrow \epsilon_t = P/k$

Let $kW =$ Power in kW from wattmeter reading
 $R =$ No. of revolution made by disc per sec

$$k = \text{revolution}/\text{kwh}$$

Energy recorded by meter under test / Recorded value (E_t) = $\frac{R}{k}$ kwh.

Let wattmeter reading be kW & reading of energy calculated by wattmeter.

Energy consumed by wattmeter | True Value (ϵ_t)
 $\epsilon_t = k_w \frac{k_w h}{3600}$

$$\% \text{ error} = \left[\frac{\epsilon_t - \epsilon_k}{\epsilon_t} \right] \times 100 =$$

Procedure :-

- 1) Make connection as per circuit diagram.
- 2) Decide the no. of revolution to take reading.
It should neither be too small nor be too large. keep it b/w 4-6 revolutions.

Exp No.

Date / /
Page No. _____
Shivatal

3. Keep load at minimum & switch on supply.
4. Take reading of E_f , W_f from energy meter, stopwatch & stop watch step. calc $P_2 - P_1$ error.
5. Increase load in 5-10 steps upto rated value of energy meter & take reading. Switch off supply.

Observation:-

- 1). When supply is on there is no load i.e. when loads present nature of its is called 'creep error'.
- 2) If at very high loads, it reads less it is called as "frictional error".
- 3). If at very high load meter reading is less, it may be due to "Dynamic breaking torque" required over load compensation.
- 4).

Precautions:-

- 1). Make sure connections carefully & get checked by your instructor before you switch on supply.
- 2). Take reading carefully, especially energy meter reading & stopwatch operation must be simultaneous.
- 3). Don't touch live wires.
- 4). Do not use energy meter beyond its rating.
- 5). The input voltage must be kept constant with help of auto transformer.

Teacher's Signature

Exp No.


Date / /
Page No.
Shivam

Result :-


The given 1-phase induction type energy meter is calibrated with help of standard wattmeter & stopwatch. It is found that Yr. error does not remain constant rather it varies in magnitude from no load to full load.

Teacher's Signature

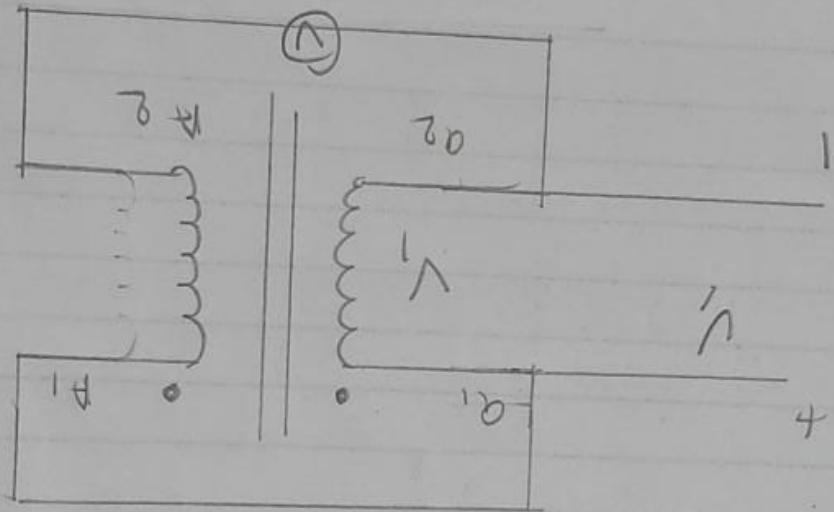Circuit diagram of full bridge test at 2.102311



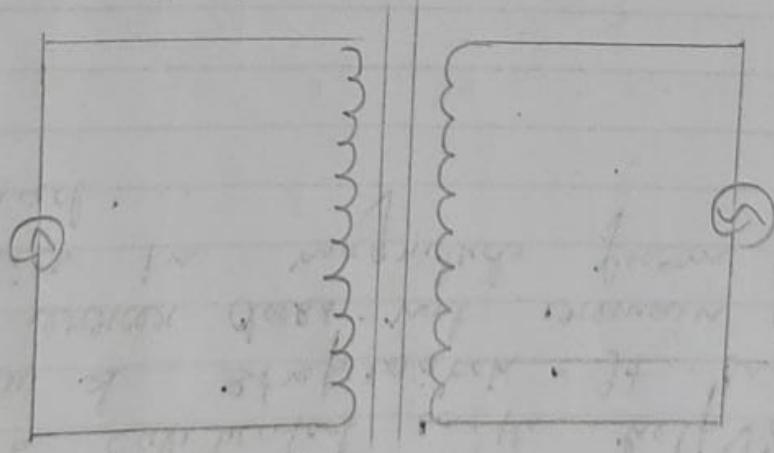Circuit Diagram for voltage ratio terminals



S.No.	Equipments	Single phase	Three phase	Three phase	Three phase	Three phase	Three phase
1.	Generator	1kVA, 230V/230V	1kVA, 230V/230V	1kVA, 230V/230V	1kVA, 230V/230V	1kVA, 230V/230V	1kVA, 230V/230V
2.	Transformer	(0-300), 5/15A	150/300/600V	By ammeter	150/300/600V	Ammeter	150/300/600V
3.	Ammeter	(0-300), 5/15A	150/300/600V	By ammeter	150/300/600V	MT	150/300/600V
4.	Voltmeter	(0-5-10) A, AC	(0-5-10) A, AC	MT	150/300/600V	MT	150/300/600V
5.	Lamp Bank load.	(0-150-300)V, AC	(0-150-300)V, AC	Resistive	150/300/600V	Resistive	150/300/600V

Apposta thus disengaged:

Opportunities: - Diversification at the local level creates opportunities for single channel.

5-1001 furnished by

Q) All components used should do what for a better output?

Answer :-

8) Which all AC-supply
A) Resistors load to some by splitting of loads equally
B) Inductors of inductance 120 - 1235 for each user.
C) Load splitting in two more difficult to the
D) Increase in current in step of 10%. If total
E) If the load from WH 220V & 110V
F) Seven days idle.


9) Solution in certain loops in loop in which
load such that second coil should not exceed
load + the open 10% of total current

10) Use E. In the of secondary winding should not exceed
no less than the primary winding as stated in
until we take in dual function load should not exceed
one half of the through current - three fourths

11) What component in full circuit diagram.
12) Which switch is in series with open so
that load is zero to measure no load
13) How to increase voltage through out - through
variable.

Answer :-

Circuit diagram for 9-1 transformer

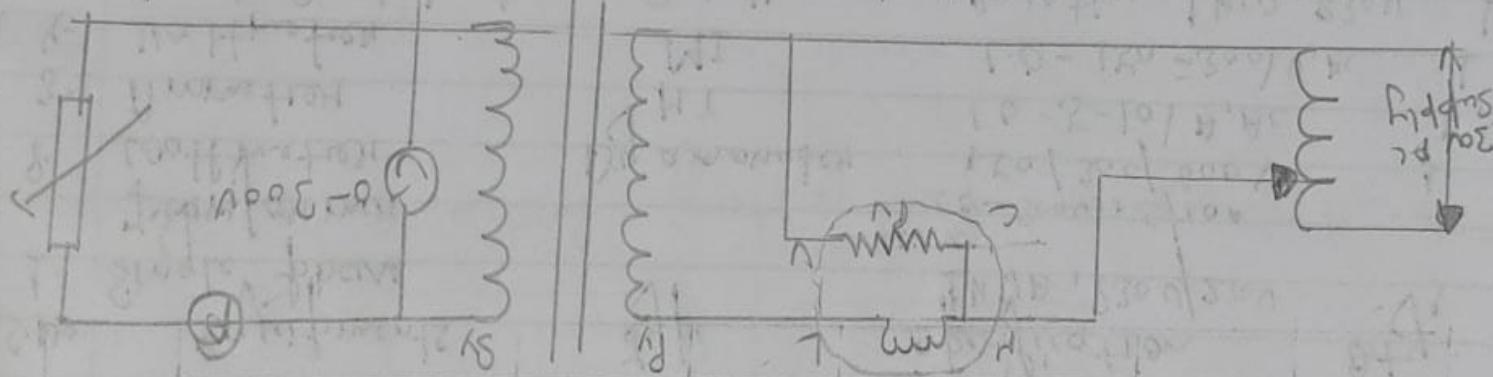

N_2/N_1	E_2	U_2	I^2	$R_2 = U_2^2/I^2$	ω_2	(V)	(A)	(W)	(V)	(A)	(W)
4.	125x2	230	214	1.5	321						
6.	245x2	490	28	2.4	4952	9.0	76	704	280	204	3.45
8.	360x2	680	230	3.6	765	10.6	90	825	280	204	3.45
10.	440x2	870	198	4.4	870	15.8	100	980	280	204	3.45

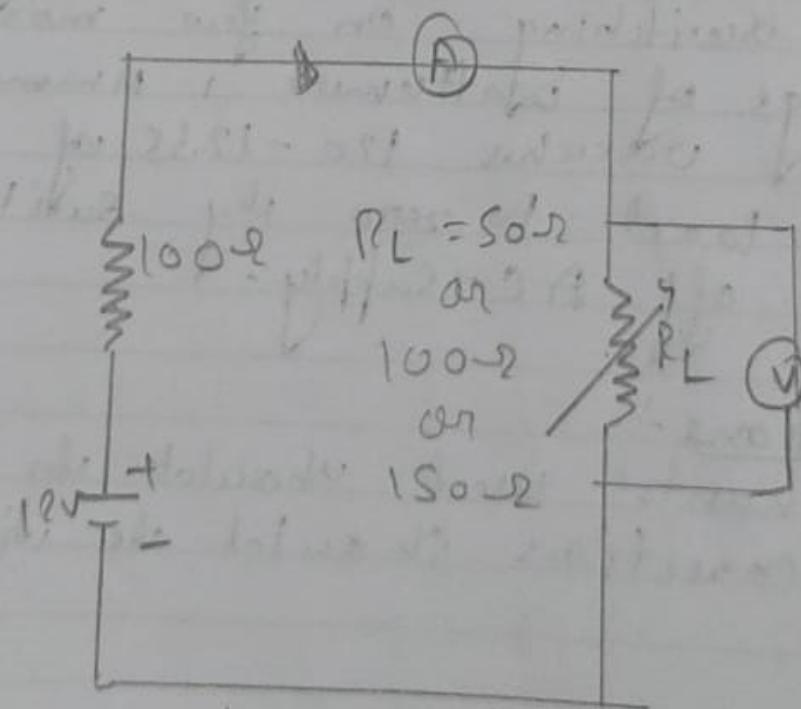
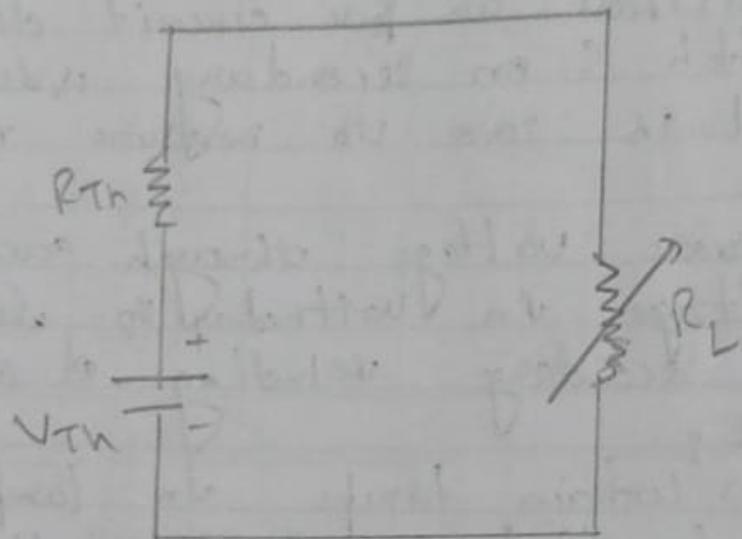


Fig :- 1

Experiment No. 10

Objective:- Verification of maximum power transfer theorem (MPT) ✓

Apparatus used:-

S.No.	Instrument	Type	Range	Dig.
1.	Supply	DC	0-12 V	1
2.	Experimental Board.		0-5 V	1
3.	Voltmeter	MG	0-5 V	1
4.	Ammeter	MG	0-10 mA	1
5.	Resistance	CRR/MER	2.3Ω/5Ω/10Ω 100Ω/500Ω	1
6.	Connecting loads.			As required.

Theory:- This theorem states that in a DC network, a resistance load unit will abstract maximum power from a network when the load resistance is equal to the resistance of the network as viewed from the output terminals with all energy sources replaced by their internal resistance.

$$P_0 = P_{\max} \text{ when } R_L = R_T = R_{TH}$$

$$\left[P_{\max} = \frac{U_{TH}^2}{4R_L} \right]$$

Teacher's Signature

Calculation

$$\textcircled{1} \quad V_{TH} = 12V, R_{TH} = 100\Omega$$

$$P_{max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{12 \times 12}{4 \times 100} = 0.36W$$

$$\textcircled{2} \quad 50\Omega \boxed{I = 75mA \text{ or } 0.075A \quad V = 4V}$$

$$P = VI = 300 = 0.3W$$

$$P_{max} = \frac{V_{TH}^2}{4R_L} = 12 \times 12 / 4 \times 50 = 0.72W$$

$$\textcircled{3} \quad 100\Omega \boxed{I = 60mA \text{ or } 0.06A \quad V = 6V}$$

$$P = VI = 360 = 0.36W$$

$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{12 \times 12}{4 \times 100} = 0.36W$$

$$\textcircled{4} \quad 150\Omega \quad I = 45mA \text{ or } V = 7.5V$$

$$P = VI = 397.5 = 0.3415W$$

$$P_{max} = \frac{V_{TH}^2}{4R_L} = \frac{12 \times 12}{4 \times 150} = 0.24W$$

$$P_{avg} = \frac{0.72 + 0.36 + 0.34}{3} = 0.44W$$

$$\Rightarrow \frac{1.38}{3} = 0.44W$$

Observation Table

S.No	R _L (Ω)	I (mA)	V Levels	R = V _E	R _{Th} (Ω)	V _m / V _e	P _{max} = $(V_T)^2 / 4R$
1	50Ω	75mA	4 volt	0.3W			0.72W
2	100Ω	60mA	6 volt	0.36W	100Ω	12V	0.36W
3	150Ω	45mA	7.5 volt	0.3375 volt			0.24W

Procedure:

- (i) Connect the circuit acc. to the fig 1.
- (ii) Select the different values of R_L (W) as — 50, 80, 100, 120, R_L (Ω)
- (iii) Note down the reading of voltmeter to find V (volts)
- (iv) Note down the reading of ammeter to find I (mA).

Precaution:-

Do not make interconnection on the board with mains switch ON.

As soon as mains is ON, the reading in the meters must be zero. If the reading in the meters is not zero, check meters.

Result:-

From the observation table, we can observe that power delivered is maximum when the load resistance is equal to int. resistance and the max value of Power is — $P_{max} = 0.44W$