

## Basic laws

① Ohm's law

② Kirchhoff's laws

→ Resisting flow of electric charge

physical current

property or ability to resist flow of current is resistance. ( $R$ ).

$$R = \frac{V}{I}$$

$\Omega$  (ohm)

→ Ohm's law → It states that voltage across a resistor is directly proportional to current  $i$  flowing through resistor.

to current  $i$

$$V \propto i$$

$$V = iR$$

$$\boxed{V = IR}$$

→ Kirchhoff's Laws →

In a lumped electric circuit for any of its node and at time  $t$ .

① Kirchhoff's current law

② Kirchhoff's voltage law

It states that the algebraic sum of currents entering a node is zero.

① KCL

Branch


$$\sum_{n=1}^N i_n = 0$$

node


\* It always define


$N$  → Number of branch connected to Node

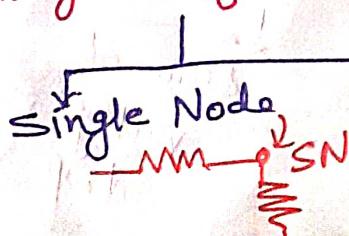$i_n$  →  $n$ th current entering or leaving Node.



Principle node

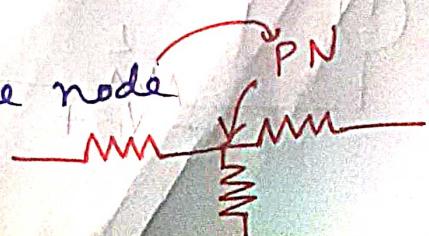


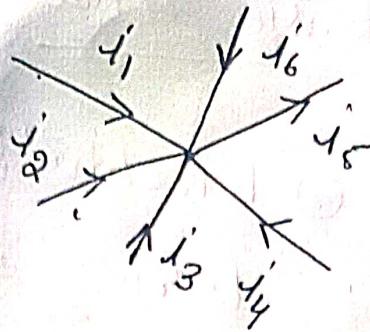

Entering Node :-  $i_1, i_2, i_6, i_3, i_4$

leaving Node :-  $i_5$

$$i_1 + i_2 + i_6 + i_3 + i_4 = i_5$$

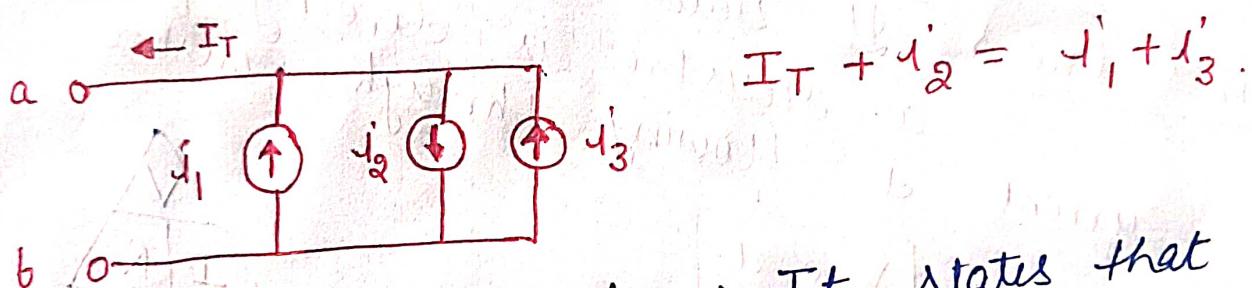


Kirchhoff's Voltage Law  $\rightarrow$  It states that algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M V_m = 0$$

$M$  = no of voltages in the loop  
or  
No of Branches in the loop.

$V_m$  = m<sup>th</sup> voltage.

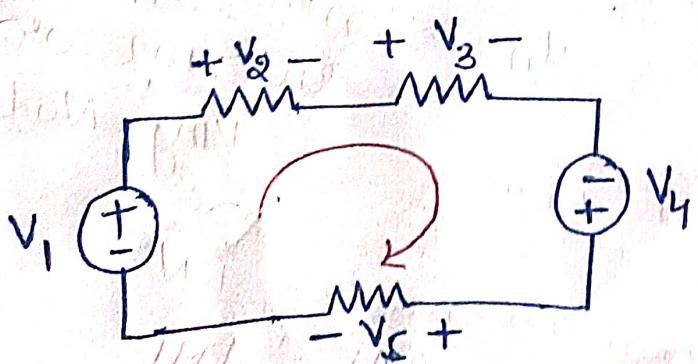

$$-V_1 + V_2 + V_3 - V_4 + V_5 = 0$$


$$V_2 + V_3 + V_5 = V_1 + V_4$$

sum of voltage drop

sum of voltage rise
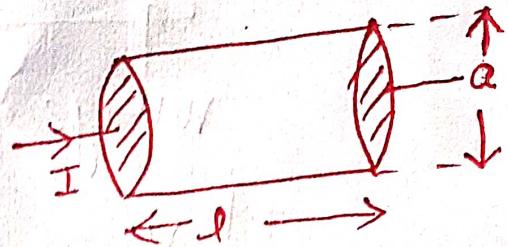
## Ohm's Law →

- \* At Constant Temperature current density is directly proportional to Electric field Intensity.



- \* At Constant temperature, potential difference across the element is directly proportional to current flowing into element.
- current density  $J = \frac{I}{A}$

$$\text{Electric field Intensity} = \frac{V}{l} \frac{\text{volts}}{\text{m.}}$$

$$(E)$$

$$\alpha = \frac{1}{l} \text{ mho/m.}$$

$$R = \rho l / A$$

By Ohm's Law →

$$\boxed{J = \alpha E}$$

$$\frac{I}{A} = \frac{1}{\rho} \cdot \frac{V}{l}$$

$$\boxed{* * *} \quad \boxed{\frac{V}{I} = \frac{\rho l}{A} = R.}$$


$$V \propto I$$

↓  
voltage drop

current

$$V = RI$$

$$\frac{V}{I} = R = \text{constant}$$

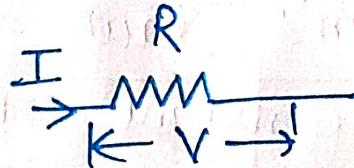

Result


Forms of ohm law :-

$$J = \alpha E$$

$$V = RI$$

$$V = R \cdot \frac{dq}{dt}$$

Note :-  $I \propto V_s$

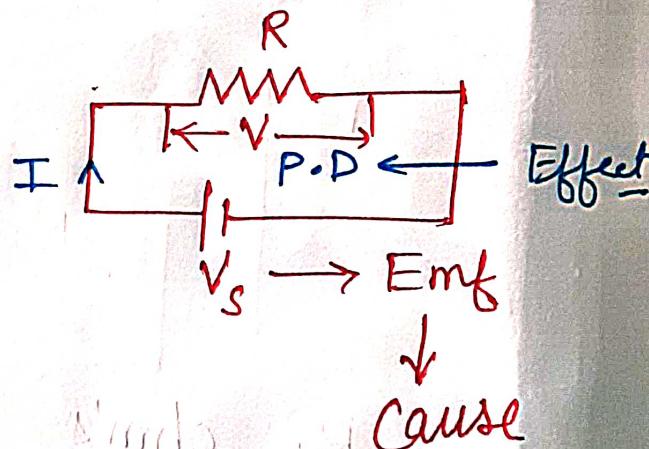

→ Emf is independent of current and Resistance Magnitude.

→ Potential difference depends upon current and Resistance Magnitude.

$$I \propto V_s$$


↑  
dependent      ↑  
Independent

EMF

$$V \propto I$$

↑  
P.D / drop  
↓  
V

(3)

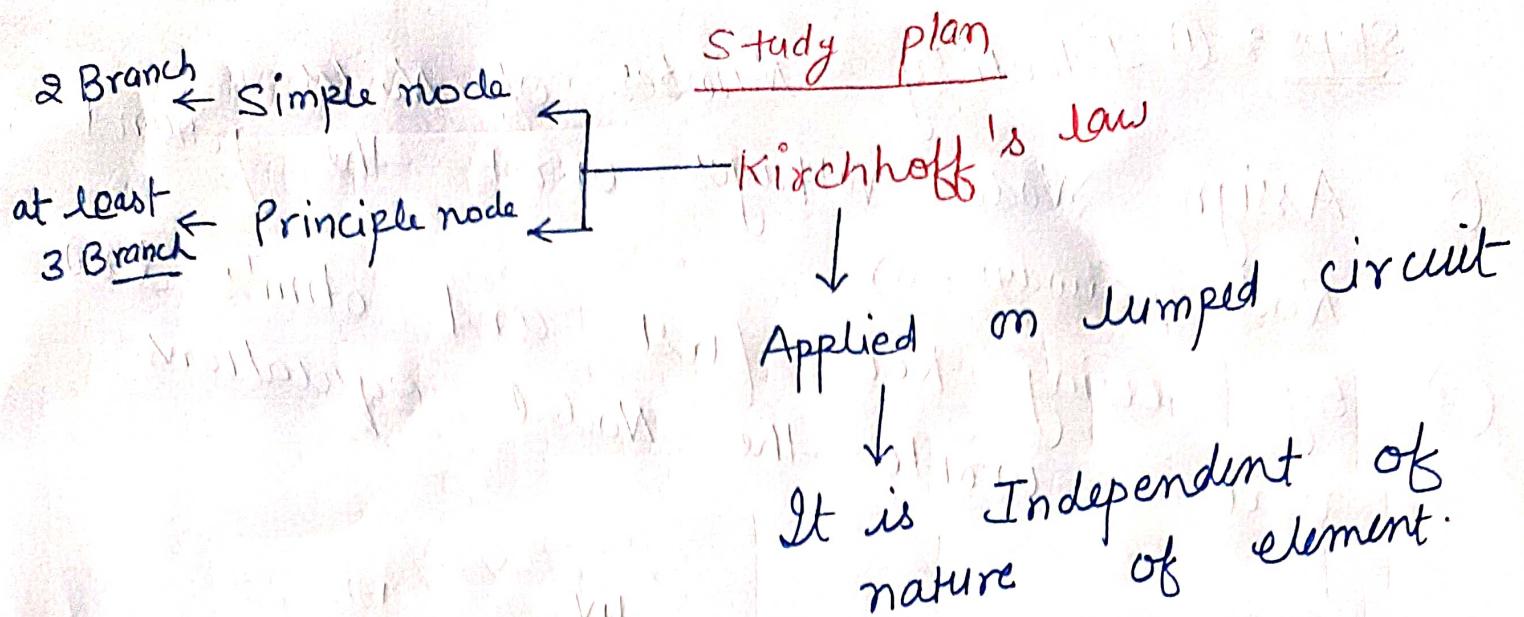

### Nodal & Mesh Analysis

Nodal → KCL + Ohm's law.

Mesh → KVL + Ohm's law.

→ Lumped circuit (KCL & KVL valid)

→ If Temperature constant (Ohm's law valid)

→ Nodal & Mesh Independent Method as  
KCL & KVL are Independent

→ Ohm's law → R, L, C (Lumped or distributed elements)

KCL & KVL → only for Lumped electric circuits (Nodal)

→ Ohm's law → Not applicable for active elements.

Valid →

Network + EMPT

KCL → Network

Not applicable for sources  
∴ V, I nature is non linear.


only applicable linear passive elements R, L, C.

(4)

KCL

- Based on conservation of charge
  - Current is rate of change of charge.
  - Since charge is constant, current is zero.
  - According to KCL, across any node sum of currents is zero.
- $I = \text{rate of change of charge}$
- $$I = \frac{dq}{dt}$$
- charge is constant
- $$I = \frac{d}{dt} (\text{constant})$$
- $I = 0$

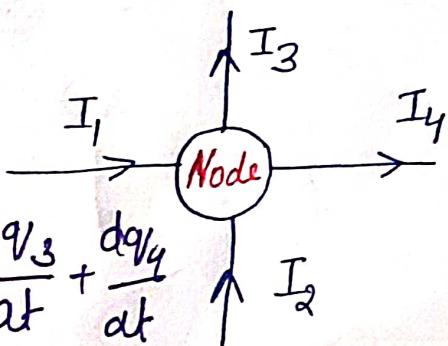- If Incoming current is taken as positive then outgoing current will be taken as negative and vice-versa.



Incoming = +ve  
outgoing = -ve.

$$*\frac{d\varphi_1}{dt} + \frac{d\varphi_2}{dt} = \frac{d\varphi_3}{dt} + \frac{d\varphi_4}{dt}$$

$\varphi_1 + \varphi_2 = \varphi_3 + \varphi_4$

Conservation of charge

$$I_1 + I_2 - I_3 - I_4 = 0$$

$$I_1 + I_2 = \underline{\underline{I_3 + I_4}}$$

Incoming current at Node      outgoing current

(5)


## Nodal Analysis

Nodal Analysis =  $\frac{V}{KCL}$  + applicable anywhere

ohm's law  
 ↓  
 Linear, Bilateral  
 Passive, lumped  
 parameter.  
 Temperature  
 = constant.


### ① Some Important Circuits :-

Two Current Sources Connected in Series.

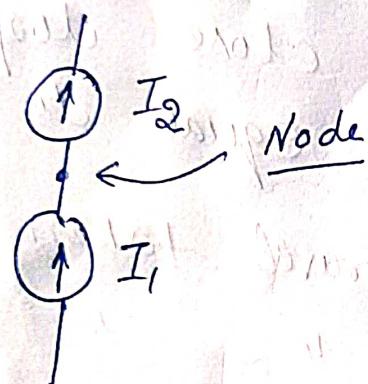

Apply KCL

$$I_1 = I_2$$


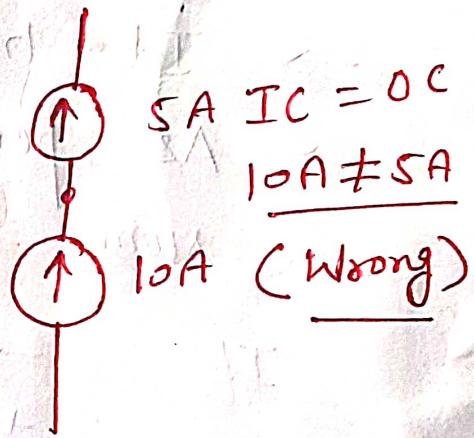


$$SA \quad IC = 0C$$


$$10A \neq SA$$

10A (Wrong)

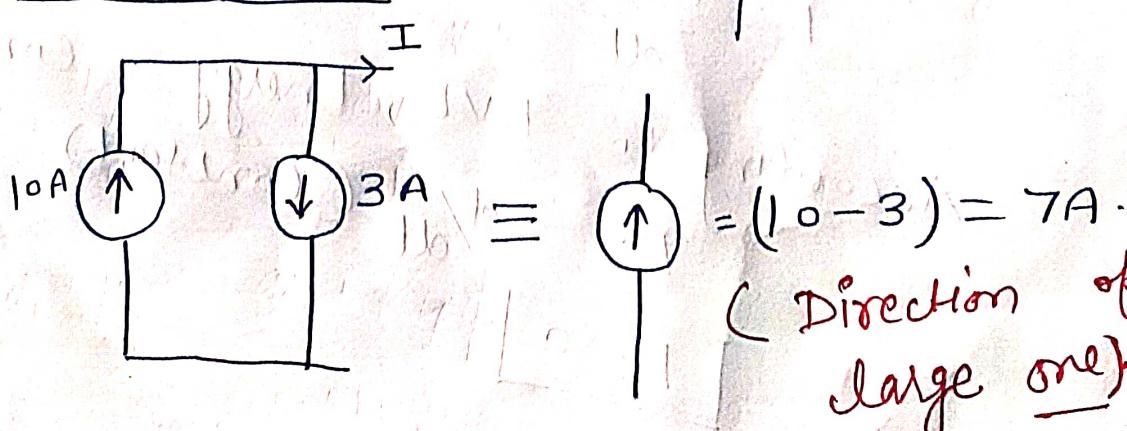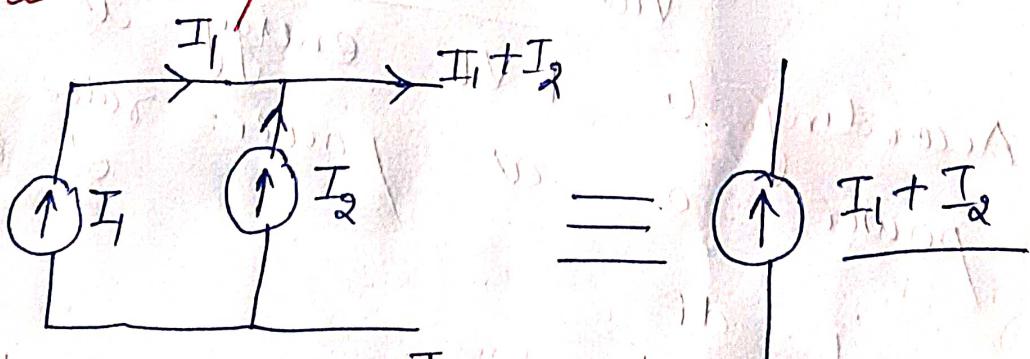② When Two Current sources are in parallel  $\rightarrow$



(Direction of large one)

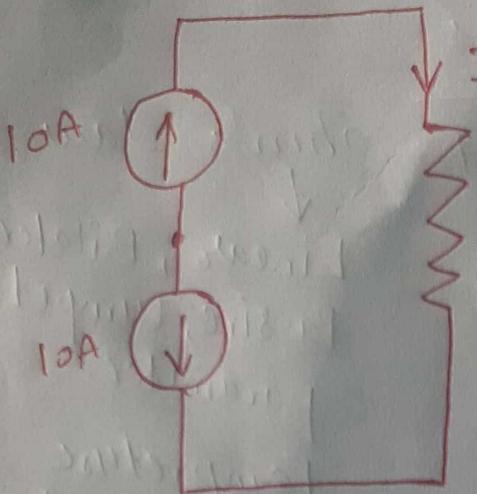

→ Not satisfy KCL  
→ circuit is wrong.

### KVL

- It based on conservation of energy.
- As per KVL, across close loop sum of voltage is equal to zero.

If      -ve to +ve      travel taken = -ve  
 +ve to -ve      "      "      = +ve

OR  
Vice - Versa.

- \* According to KVL energy is constant.
- \* power = 0 as power = rate of change of energy


$$P = \frac{dE}{dt}$$

According to KVL, Energy = Constant

$$P = \frac{d}{dt} \text{ (Constant)}$$

$P = 0$

(6)

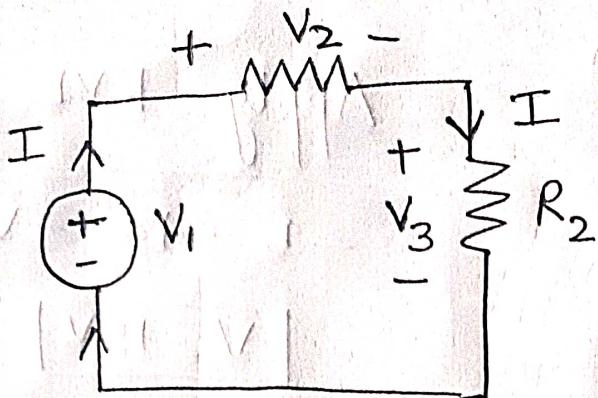

$$-V_1 + V_2 + V_3 = 0$$

$$V_V = V_2 + V_3$$

-ve to +ve = Negative  
+ve to -ve = positive

$$-\frac{dw_1}{dq} + \frac{dw_2}{dq} + \frac{dw_3}{dq} = 0$$


$$-w_1 + w_2 + w_3 = 0$$

Conservation of

Mesh Analysis = KVL + Ohm's law


Mesh Analysis = ① Linear ② Bilateral  
③ Passive ④ Temperature

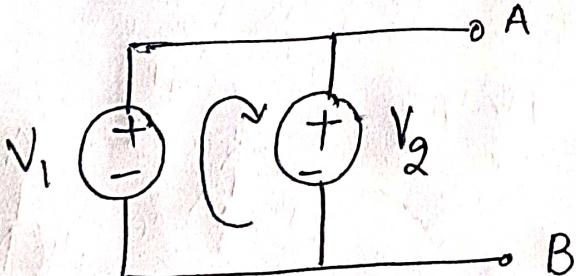Case 1 → Two voltage source connected in parallel :-




$$-V_1 + V_2 = 0$$


$$V_1 = V_2$$

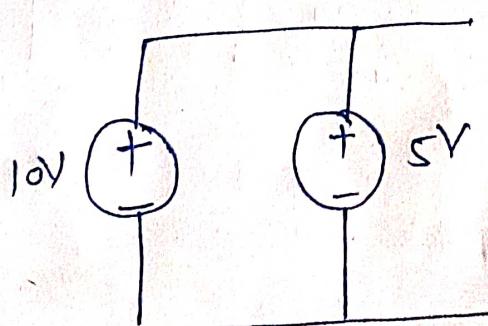

← Wrong

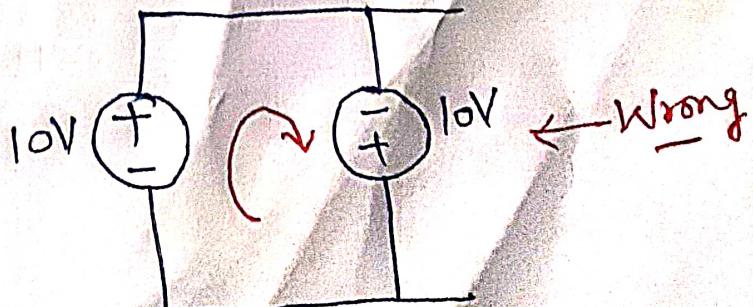

← Wrong

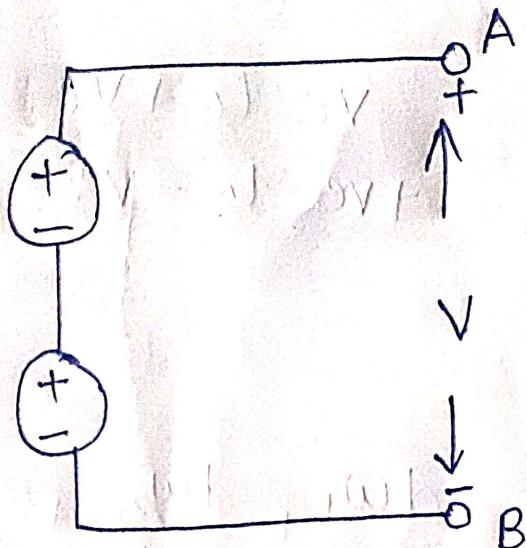


Apply KVL  $\rightarrow$

$$-5 - 10 + V = 0$$

$$V = 15V$$

15V

Polarity

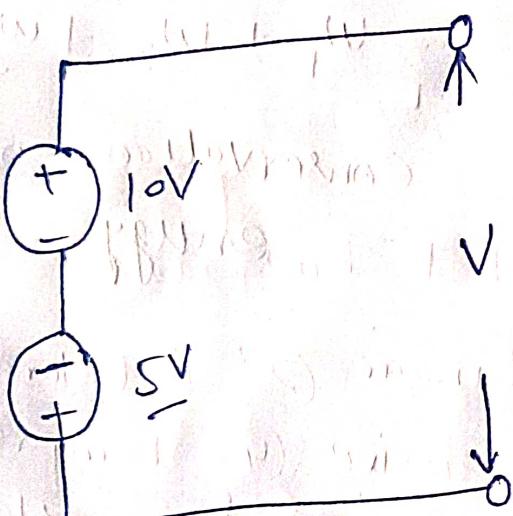

Apply KVL  $\rightarrow$

$$+5V - 10V + V = 0$$

$$V = 5V$$



## MESH AND NODAL ANALYSIS

- Basic Techniques used in finding solutions of a network.
- Two Basic Circuit analysis techniques
  - Nodal Analysis → KCL + ohm's law
  - Mesh Analysis → KVL + ohm's law
- MESH Analysis:- Based upon KVL.

Step 1 → Inspect total number of mesh in the circuit. (All Independent closed path)

Step 2 → Label the mesh current in any arbitrary direction in each mesh.

Step 3 → Put the sign convention across each element.


→ Current Entering side across a resistor is marked as positive.

→ Current leaving side marked as negative.

Step 4 → Apply KVL at each Mesh.

Note → ① The common branch carries the algebraic sum of mesh currents flowing through it.

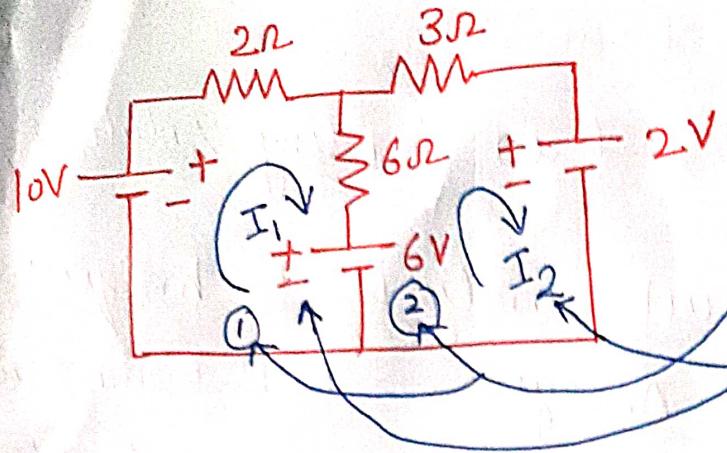② No of Equations = No of Unknowns  
Solve equations and determine mesh current.




① Inspect Mesh

i.e. = 2.

Total Mesh = 2

② Label Mesh current either clockwise or Anticlockwise (prefer clockwise)

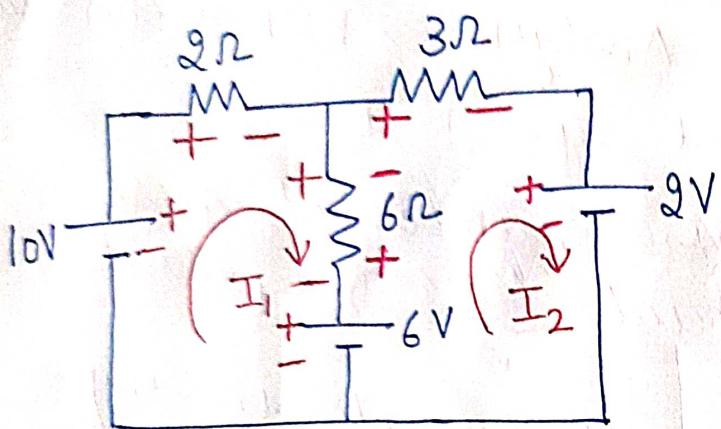③ Put sign convention across each element.



Loop ① →

$$-10 + 2I_1 + 6(I_1 - I_2) + 6 = 0$$

$$\therefore 2I_1 + 6I_1 - 6I_2 = 4$$

$$8I_1 - 6I_2 = 4 \quad \text{①}$$

Loop ② →

$$-6 + 6(I_2 - I_1) + 3I_2 + 2 = 0$$

$$9I_2 - 6I_1 = 4 \quad \text{②}$$

④ Apply KVL at each Mesh

⑤ Solve these equations

$$8I_1 - 6I_2 = 4 \times 6$$

$$9I_2 - 6I_1 = 4 \times 8$$

$$48I_1 - 36I_2 = 24$$

$$-48I_1 + 72I_2 = 32$$

$$+36I_2 = 56$$

$$I_2 = \frac{-8}{36} = \frac{2}{9}$$

$$8I_1 + \frac{4}{3} = 4$$

$$8I_1 = \frac{8}{3}$$

$$I_1 = \frac{1}{3} = 0.33A$$

$$8I_1 - \frac{2}{3} \times \frac{14}{9} = 4$$

$$8I_1 = 4 + \frac{28}{27}$$

$$I_1 = \frac{40}{3} \times \frac{1}{27} = \frac{5}{3} = 1.667A$$

BASED ON CONCEPT NODAL & MESH (2)


Numericals

Q:- Determine the current in all the branches of Network using Loop Analysis.

Loop Analysis :- Loop 1 →

$$-30 + 4I_1 + 2(I_1 + I_2) = 0$$

$$6I_1 + 2I_2 = 30 \rightarrow ①$$

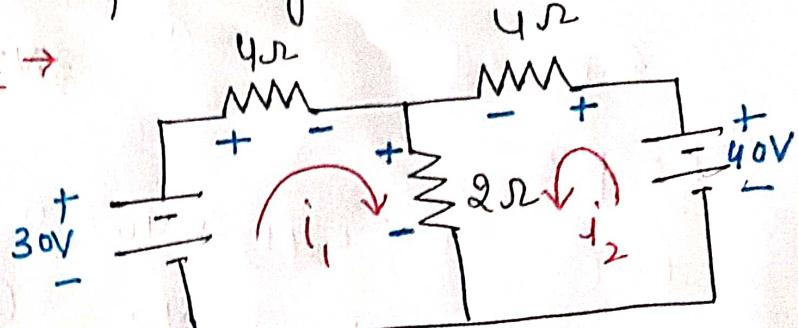

Loop 2 →

$$-40 + 4I_2 + 2(I_1 + I_2) = 0$$

$$6I_2 + 2I_1 = 40 \rightarrow ②$$

Equation ① & Equation ②

$$6I_1 + 2I_2 = 30$$

$$2I_1 + 6I_2 = 40 \times 3$$

$$\underline{6I_1 + 18I_2 = 120}$$

$$\underline{\underline{+16I_2 = +90}}$$

\*\*\*  $I_2 = \frac{90}{16} = \frac{45}{8} \text{ A}$

$$3.6 \times \frac{45}{8} + 2I_1 = 40$$

$$\underline{13.5 + 8I_1 = 160}$$

$$8I_1 = 25$$

\*\*\*  $I_1 = \frac{25}{8} \text{ A}$

Loop 1 →


$$-30 + 4I_1 + 2(I_1 - I_2) = 0$$

$$6I_1 - 2I_2 = 30 \rightarrow ①$$

Loop 2 →

$$+2(I_2 - I_1) + 4I_2 + 40 = 0$$

$$6I_2 - 2I_1 = -40 \rightarrow ②$$

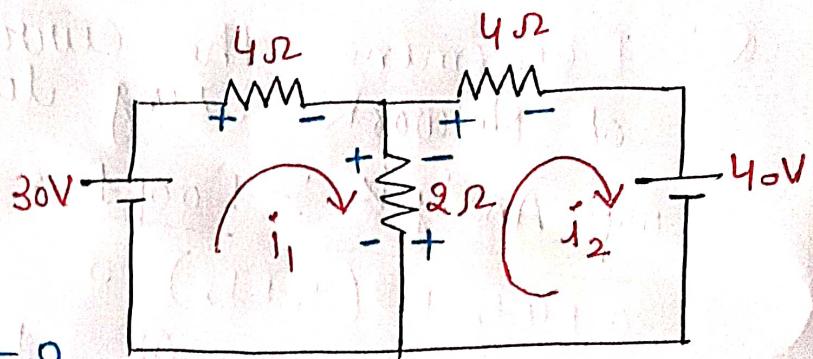

Solve equation form by equation Loop 1 & Loop 2 →

$$\begin{aligned} 6I_1 - 2I_2 &= 30 \\ -2I_1 + 6I_2 &= -40 \times 3 \\ -6I_1 + 18I_2 &= -120 \end{aligned}$$

$$I_2 = \frac{-120 + 30}{18 - 2} = \frac{-90}{16} \Rightarrow -\frac{45}{8} \text{ A}$$

\*\*\*

$$I_2 = -\frac{45}{8} \text{ A}$$

Solve for  $I_1$ , equation 1 →

$$6I_1 - 2I_2 = 30$$

put value of  $I_2$  in equation -①

$$6I_1 - 2 \times -\frac{45}{8} = 30$$

$$6I_1 = 30 + \frac{90}{8}$$

$$6I_1 = \frac{240 + 90}{8} = \frac{330}{8}$$


$$I_1 = \frac{330}{8} \times \frac{1}{6} = \frac{55}{8} = \frac{25}{4} \text{ A}$$

\* Mesh Analysis with Current Source :-

→ presence of current source reduces no of equations.
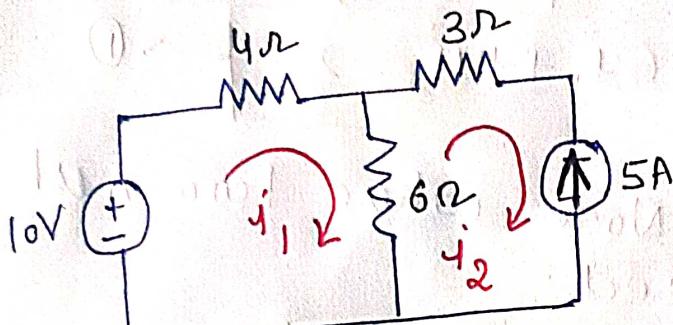
### Special Cases

Case 1 → When current source exist only in one Mesh.



$$-10 + 4i_1 + 6(i_1 - i_2) = 0$$

$$\text{But } i_2 = -5 \text{ A}$$

put in equation loop 1

$$-10 + 4i_1 + 6(i_1 + 5) = 0$$

$$-10 + 4i_1 + 6i_1 + 30 = 0$$

$$10i_1 = -20$$



$$i_1 = -2 \text{ A}$$

\*\*

Case 2 → When current source exists between two meshes.

Ex: Create a supermesh current source and element

→ By excluding the connected in series.

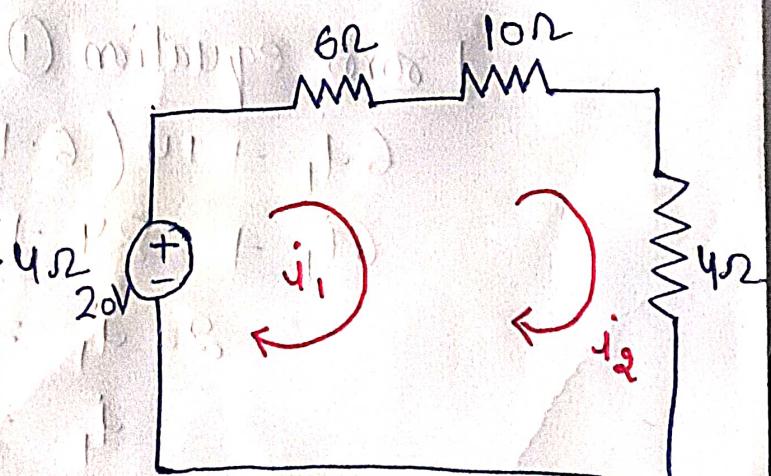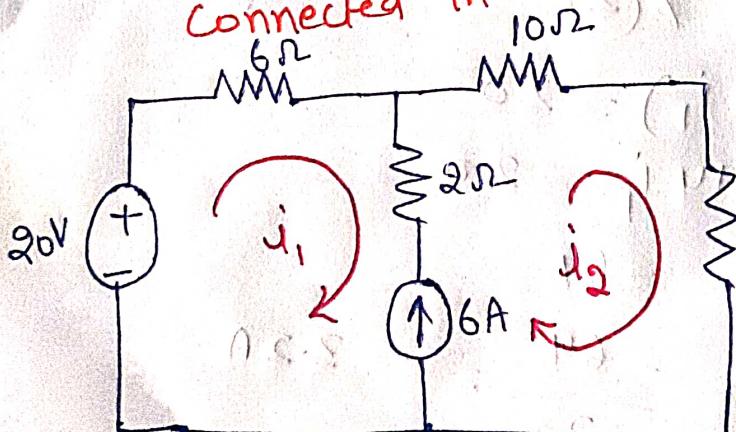


Note:- Super Mesh create when two mesh have properties of common current source.

properties of super Mesh → ① It require application of KVL & KCL.

② A supermesh has no current of its own.

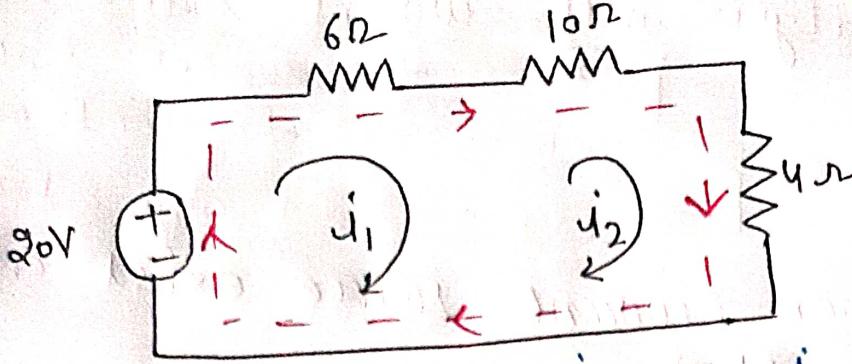③ The current source in supermesh provides constraint equation necessary to solve for Mesh Current.




Apply KVL  $\rightarrow -20 + 6i_1 + 10i_2 + 4i_2 = 0$

$$6i_1 + 14i_2 = 20 \quad (1)$$

Apply KCL  $\rightarrow$  to a Node where two mesh intersect.

Apply KCL to Node

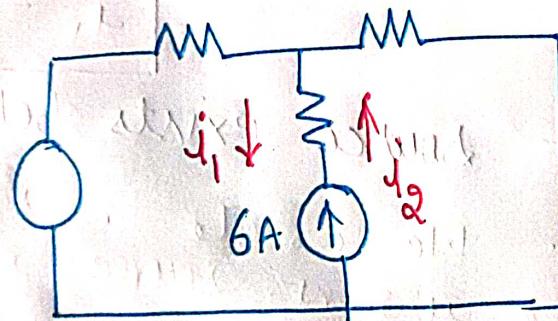

As 6A has upward direction,  
i.e  $i_2 > i_1$

$$i_2 - i_1 = 6$$

$$i_2 = 6 + i_1 \quad (2)$$

From equation (1) & (2)

$$6i_1 + 14(6 + i_1) = 20$$

$$6i_1 + (84 + 14i_1) = 20$$

$$20i_1 = -64$$

$$i_1 = \frac{-64}{20} = -3.2 \text{ A}$$

$$i_2 = 6 + i_1 \quad 2.8 \text{ A} \quad **$$

(12)

\* loop ① &amp; ③ Super Mesh

$$-10 + 4(i_1 - i_2) + 10(i_3 - i_2)$$

$$+ i_3 + 7i_3 = 0$$

$$4i_1 - 4i_2 + 10i_3 - 10i_2 + i_3 + 7i_3 = 10$$

$$4i_1 - 4i_2 + 18i_3 - 10i_2 = 10 \rightarrow ①$$

IN MESH ②


$$5i_2 + 9i_2 + 10(i_2 - i_3) + 4(i_2 - i_1) \rightarrow ②$$

$$14i_2 + 10i_2 - 10i_3 + 4i_2 - 4i_1 = 0$$

$$28i_2 - 10i_3 - 4i_1 = 0 \rightarrow ②$$

$$i_3 = i_1 + 3A$$

By applying KCL.

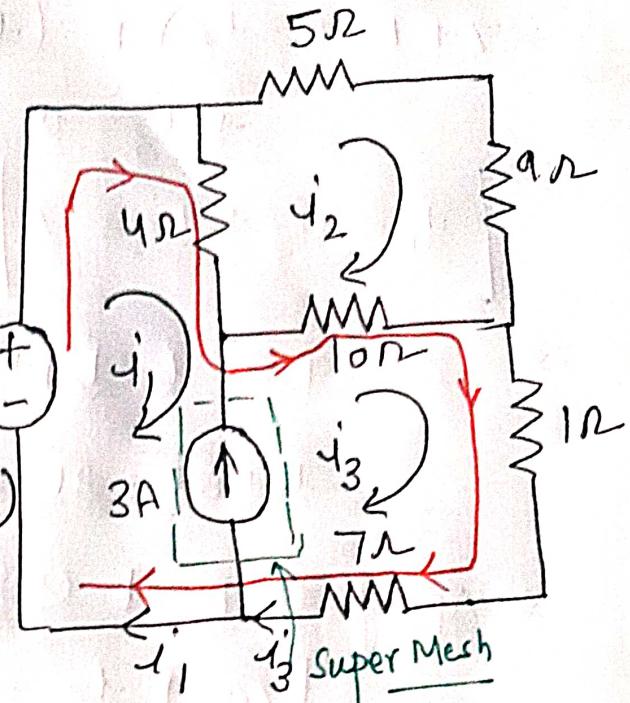Find current  $i_1$  in circuit given above.

$$28i_2 - 10(i_1 + 3) - 4i_1 = 0$$

$$28i_2 - 10i_1 - 30 - 4i_1 = 0$$

$$28i_2 - 14i_1 = 30 \rightarrow ③$$

$$4i_1 - 14i_2 + 18(i_1 + 3) = 10$$

$$4i_1 - 14i_2 + 18i_1 + 54 = 10$$

$$2 \times 22i_1 - 14i_2 = -44 = 44i_1 - 28i_2 = -88$$

$$-14i_1 + 28i_2 = 30$$

$$\underline{30i_1 = -58}$$

$$i_1 = \frac{-58}{30} \Rightarrow -1.93A$$

## \* EXAMPLE OF SUPERMESH \*

\* Mesh ① & ③ has super mesh.

$$-7 + 1(i_1 - i_2) + 3(i_3 - i_2)$$

$$+ i_3 = 0$$

$$\boxed{i_1 - 4i_2 + 4i_3 = 7} \rightarrow ①$$

\*  $2i_2 + 3(i_2 + i_3) + 1(i_2 - i_1)$   
 [Mesh-2]  
 $-i_1 + 6i_2 - 3i_3 = 0 \rightarrow ②$

\* Apply KCL at common Node

$$\boxed{7A + i_3 = i_1}$$

Put in ①

$$7 + i_3 - 4i_2 + 4i_3 = 7$$

$$5i_3 - 4i_2 = 0 \rightarrow ③$$

$$-7 - i_3 + 6i_2 + 3i_3 = 0$$


$$\begin{aligned} 6i_2 - 4i_3 &= 7 \times 4 \\ -4i_2 + 5i_3 &= 0 \times 6 \end{aligned}$$

$$\cancel{24i_2} - 16i_3 = 28$$

$$\cancel{-24i_2} + 30i_3 = 0$$

$$14i_3 = 28$$

$$\boxed{i_3 = 2A}$$

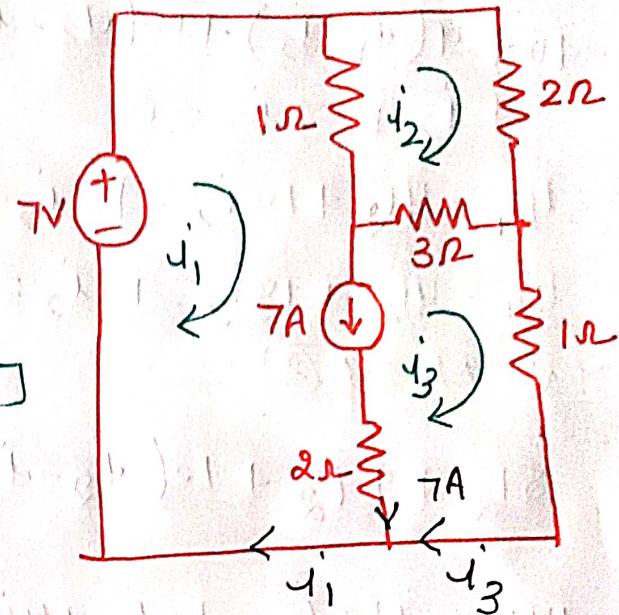


$$i_1 = 2A + 7A = 9A$$

$$9 - 4i_2 + 8 = 7$$

$$-4i_2 = -10$$

$$i_2 = \frac{10}{4} = 2.5A$$

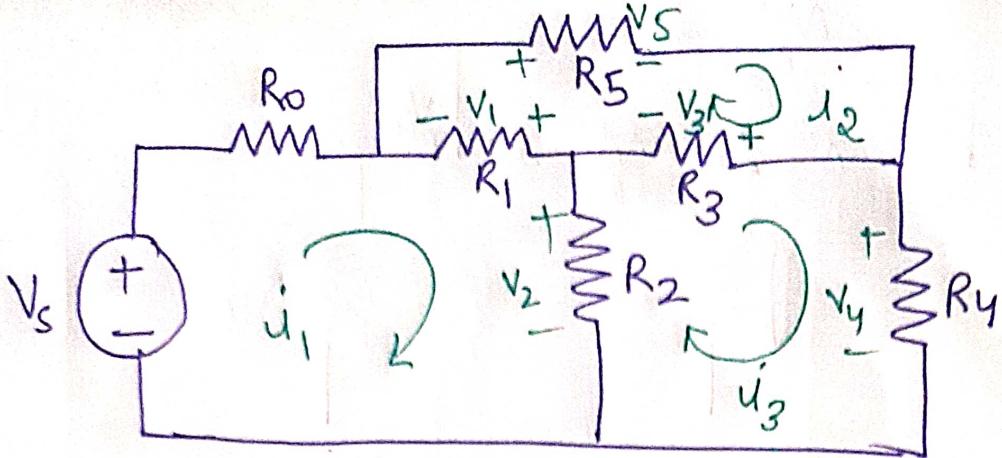

14

For Mesh 1  $\rightarrow$

$$-V_s + R_0 i_1 + R_1 (i_1 - i_2) + R_0 (i_1 - i_3) = 0 \quad ①$$

For Mesh 2  $\rightarrow$

$$+ i_2 R_5 + R_3 (i_2 - i_3) + R_1 (i_2 - i_1) = 0 \quad ②$$


For Mesh 3  $\rightarrow$

$$+ R_4 i_3 + R_2 (i_3 - i_1) + R_3 (i_3 - i_2) = 0 \quad ③$$

$$V_s = i_1 (R_0 + R_1 + R_2) - R_1 i_2 - R_2 i_3 = 0$$

$$0 = i_2 (R_5 + R_3 + R_1) - R_3 i_3 - R_1 i_1 = 0$$
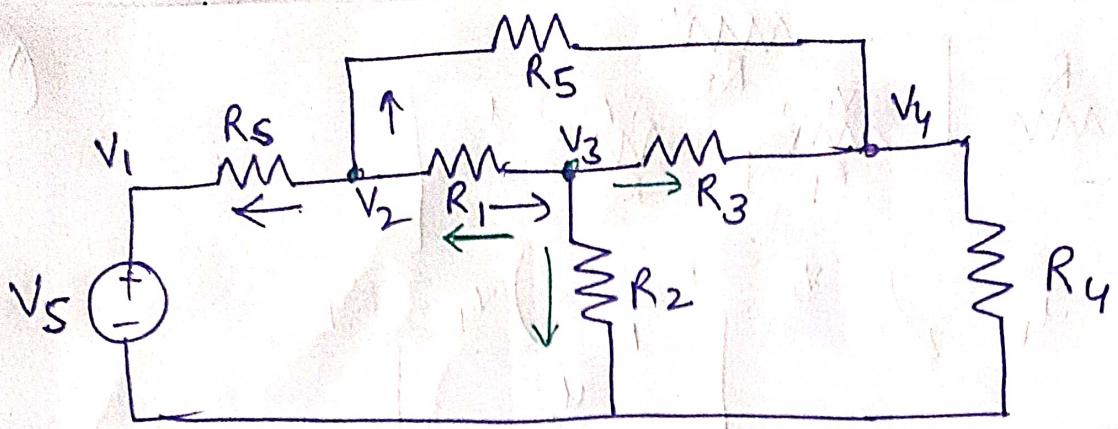
$$0 = i_3 (R_4 + R_2 + R_3) - i_1 R_2 - i_2 R_3 = 0$$



$$IR_1 = \frac{V_3 - V_2}{R_1}$$

$$IR_2 = \frac{V_3}{R_2}$$

$$IR_3 = \frac{V_3 - V_4}{R_3}$$

$$IR_1 + IR_2 + IR_3 = 0$$

$$\frac{V_3 - V_2}{R_1} + \frac{V_3}{R_2} + \frac{V_3 - V_4}{R_3} = 0$$

$$\frac{V_2 - V_S}{R_S} + \frac{V_2 - V_3}{R_1} + \frac{V_2 - V_4}{R_S} = 0$$

$$\frac{V_4 - V_3}{R_3} + \frac{V_4 - V_2}{R_S} + \frac{V_4}{R_4} = 0$$

$$\left( \frac{1}{R_S} + \frac{1}{R_1} + \frac{1}{R_S} \right) V_2 - \frac{V_3}{R_1} - \frac{V_4}{R_S} = \frac{V_S}{R_S} \rightarrow ①$$

$$-\frac{V_2}{R_1} + \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_3 - \frac{V_4}{R_3} = 0$$

$$-\frac{V_2}{R_S} - \frac{V_3}{R_3} + \left( \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_S} \right) V_4 = 0$$

(13)

Nodal Analysis  $\rightarrow$  KCL + Ohm's law

Step I  $\rightarrow$  Inspect the total number of nodes in the circuit.

$\rightarrow$  Select one Node as reference Node.  
 $\rightarrow$  Label the Remaining Node as unknown node voltages w.r.t the reference node [datum or ground].

Step-II  $\rightarrow$  Assign Branch currents in each element (Branch). [The choice of direction is arbitrary.]

Step-III  $\rightarrow$  Write standard form of Node equations (KCL) by inspecting the circuit.

Step-IV  $\rightarrow$  Express the branch currents in terms of Node assigned voltages.


Step V  $\rightarrow$  Solve a set of simultaneous algebraic equation for Node voltages and ultimately the current.

$$i = \frac{V_{\text{higher}} - V_{\text{lower}}}{R}$$

→ current flow from higher potential to lower potential in a resistor.

Q1 → Consider Network shown in below figure

Find  $V_a$ .

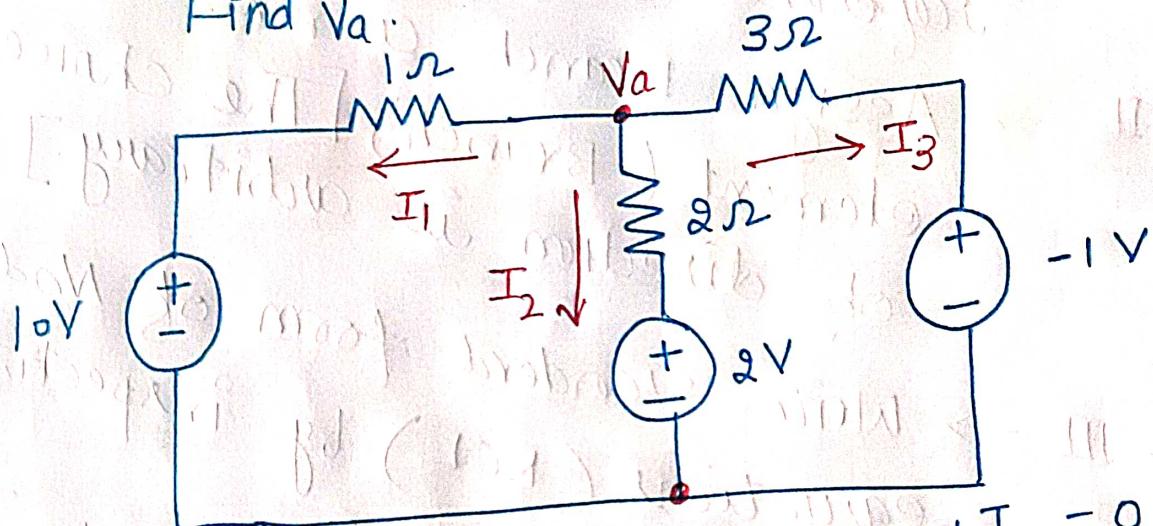

At  $V_a$  apply KCL  $\rightarrow I_1 + I_2 + I_3 = 0$

$$\frac{V_a - 10}{1} + \frac{V_a - 2}{2} + \frac{V_a - (-1)}{3} = 0$$

$$\frac{6V_a - 60 + 3V_a - 6 + 2V_a + 2}{6} = 0$$

$$11V_a = 64$$

$$V_a = \frac{64}{11} = 5.82V$$

(Q)

By Nodal Analysis →

Apply KCL at Node  $V_a$  →

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_a - 30}{4} + \frac{V_a}{2} + \frac{V_a - 40}{4} = 0$$


$$V_a - 30 + 2V_a + V_a - 40 = 0$$

$$4V_a - 70 = 0$$

$$V_a = \frac{+70}{4} = \underline{17.50 \text{ V}}$$


$$I_1 = \frac{17.50 \text{ V} - 30 \text{ V}}{4} = \frac{-12.50}{4} = -\frac{25}{8} \text{ A}$$
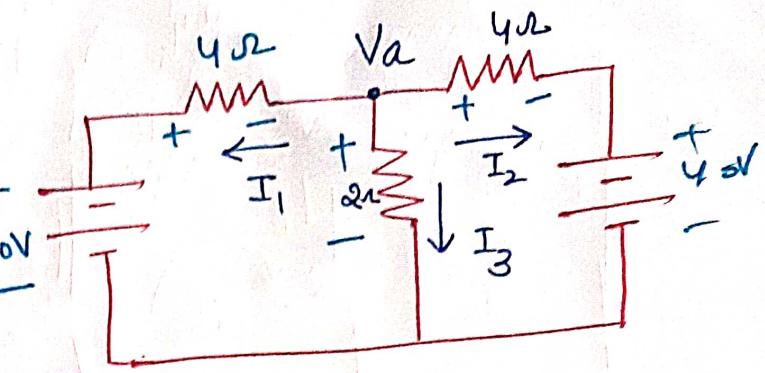
$$I_2 = \frac{17.50 - 40 \text{ V}}{4} = \frac{22.50}{4} = -\frac{45}{8} \text{ A}$$



(10)

### \* Mesh Analysis \*

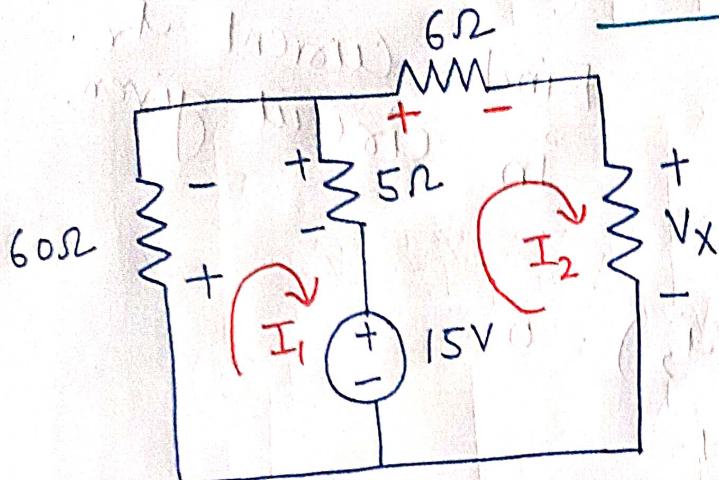

Find Voltage  $V_x$

in given figure.

For loop 1  $\rightarrow 60I_1 + 5(I_1 - I_2) + 15V = 0$

$$65I_1 - 5I_2 = -15V \quad \text{---} (1)$$

For loop 2  $\rightarrow -15 + 17I_2 - 5I_1 = 0$


$$17I_2 - 5I_1 = 15 \quad \text{---} (2)$$

$$\begin{aligned} 65I_1 - 5I_2 &= -15 \\ -5I_1 + 17I_2 &= 15 \times 13 \\ -65I_1 + 17 \times 13I_2 &= 195 \end{aligned}$$

$$(221 - 5)I_2 = 195 - 15$$

$$I_2 = \frac{180}{216} = \frac{90}{108} = \frac{5}{6}$$

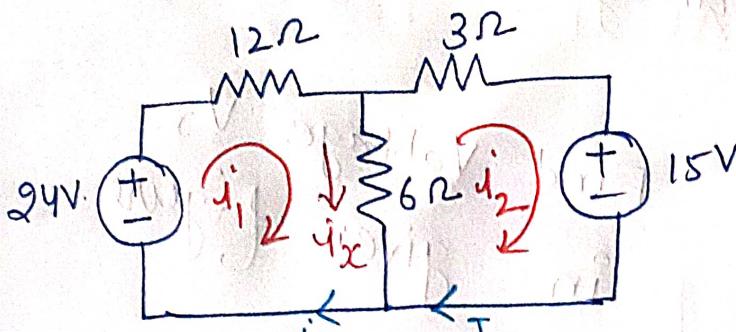\*\*\*  $V_x = I_2 R = I_2 \times 6\Omega = \frac{5}{6} \times 6\Omega = 5V$



Find current  $i_x$  in circuit given.

$$\text{Loop 1} \rightarrow -24 + 12i_1 + 6(i_1 - i_2) = 0$$

$$18i_1 - 6i_2 = 24$$

$$3i_1 - 2i_2 = 4 \quad \boxed{\textcircled{1}}$$

$$\text{Loop 2} \rightarrow 6(I_2 - I_1) + 3I_2 + 15 = 0$$

$$9I_2 - 6I_1 = -15 \quad \boxed{\textcircled{2}}$$

$$-I_2 + 3i_1 = 4 \times 2 = -2I_2 + 6I_1 = 8$$

$$9I_2 - 6i_1 = -15$$

$$7I_2 = -7$$

$$I_2 = -1 \quad \boxed{\textcircled{3}}$$

Put value of  $I_2$  in equation  $\textcircled{1}$

$$3i_1 + 1 = 4$$

$$3i_1 = 3$$


$$i_1 = 1 \quad \boxed{\textcircled{4}}$$

According to loop.  $I_x = I_1 - I_2$

$$I_x = 1 - (-1) = 2$$

$$I_x = 2 \text{ A} \quad \boxed{\textcircled{5}}$$

# TUTORIAL + ASSIGNMENT

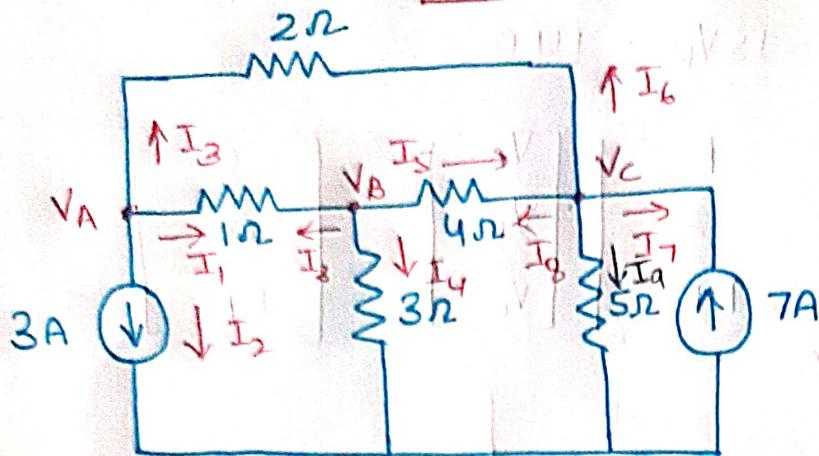

At Node  $V_A$  →

$$\text{Apply KCL} \rightarrow I_1 + I_2 + I_3 = 0$$

$$\frac{V_A - V_B}{1} + 3 + \frac{V_A - V_C}{2} = 0$$

$$2V_A - 2V_B + 6 + V_A - V_C = 0$$

$$\boxed{3V_A - 2V_B - V_C = -6} \rightarrow ①$$

At Node  $V_B$  →

$$I_3 + I_4 + I_5 = 0$$

$$\frac{V_B - V_A}{1} + \frac{V_B}{3} + \frac{V_B - V_C}{4} = 0$$

$$12V_B - 12V_A + 4V_B + 3V_B - 3V_C = 0$$

$$\boxed{19V_B - 12V_A - 3V_C = 0} \rightarrow ②$$

At Node  $V_C$  →  $I_7 + I_8 + I_6 = 0$

$$\frac{V_C}{5} + 7 + \frac{V_C - V_B}{4} + \frac{V_C - V_A}{2} = 0$$

$$\frac{4V_C - 140 + 5V_C - 5V_B + 10V_C - 10V_A}{20} = 0$$

$$\boxed{19V_C - 10V_A + 15V_B = 140} \rightarrow ③$$

$$111) 3V_A - 2V_B - V_C = -6$$

$$19V_B - 12V_A - 3V_C = 0$$

$$19V_C - 10V_A - 15V_B = 140$$

$$\left[ \begin{array}{ccc|c} 3 & -2 & 1 & -6 \\ -12 & 19 & -3 & 0 \\ -10 & -15 & 19 & 140 \end{array} \right] \xrightarrow{\Delta} \left[ \begin{array}{c|c|c|c} V_A & V_B & V_C & \\ \hline -6 & 0 & 140 \end{array} \right]$$

$$\Delta_1 = \left[ \begin{array}{ccc} -6 & -2 & 1 \\ 0 & 19 & -3 \\ 140 & -15 & 19 \end{array} \right]$$

$$\Delta_2 = \left[ \begin{array}{ccc} 3 & -6 & 1 \\ -12 & 0 & -3 \\ -10 & 140 & 19 \end{array} \right]$$

$$\Delta_3 = \left[ \begin{array}{ccc} 3 & -2 & -6 \\ -12 & 19 & 0 \\ -10 & -15 & 140 \end{array} \right]$$

$$V_A = \frac{\Delta_1}{\Delta}, \quad V_B = \frac{\Delta_2}{\Delta}, \quad V_C = \frac{\Delta_3}{\Delta}$$

$$\Delta = \frac{136}{136}$$


$$V_A = \frac{712}{136} = 5.235 A$$

1b
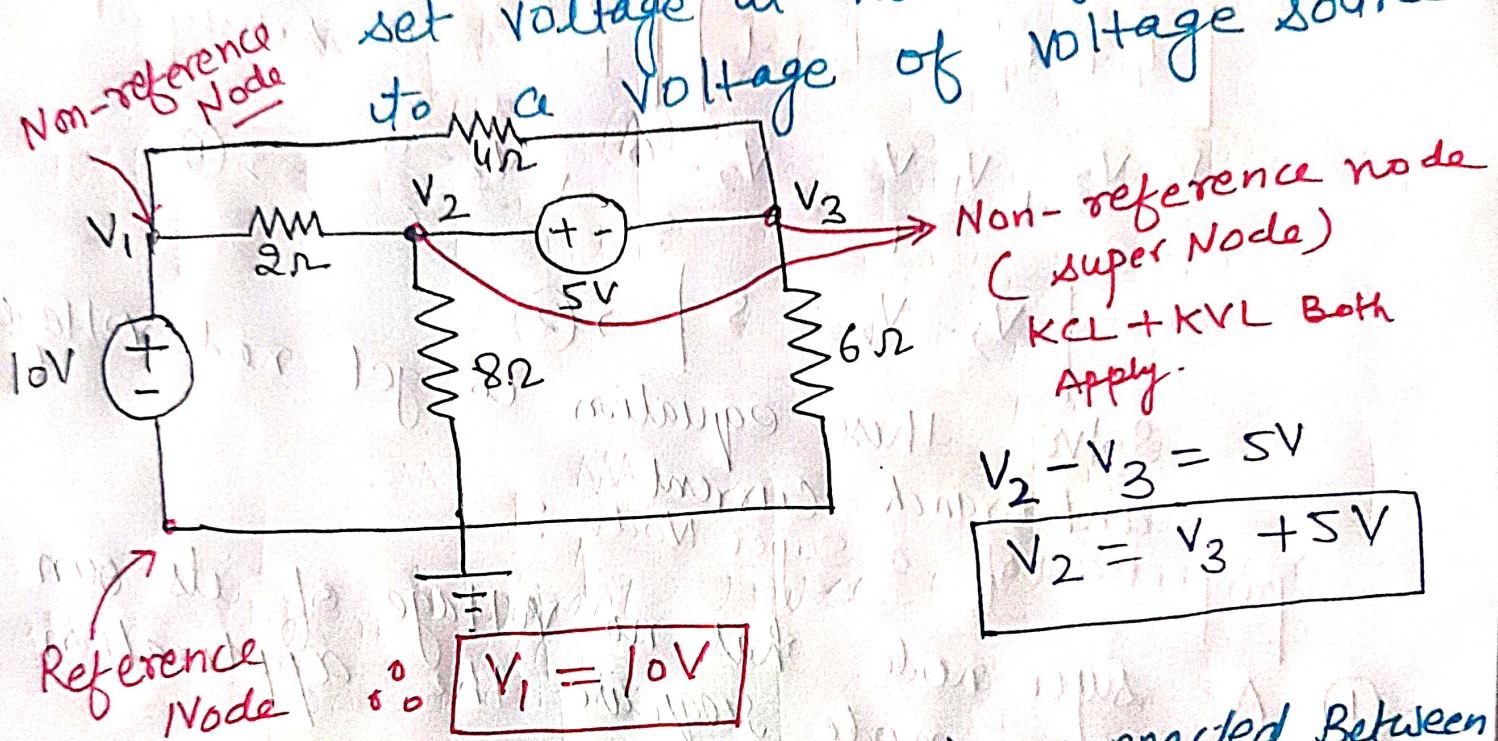
## Nodal Analysis with Voltage Sources :-


→ KCL + KVL + Ohm's law

Case 1 → If voltage source is connected between the reference node and a non-reference node, we simply set voltage at non-reference node to a voltage of voltage source.




Case 2 → If voltage source is connected between two non-reference nodes. → super Node

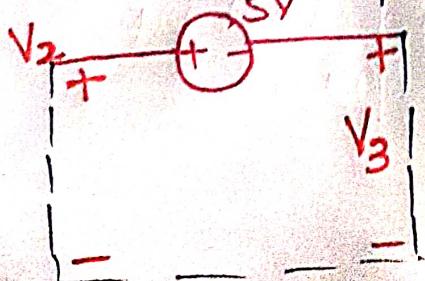Super Node :- It is formed by enclosing a voltage source connected between two non-reference nodes and any elements connected in parallel with it.



$$-V_2 + 5V + V_3 = 0$$

$$V_2 = V_3 + 5V$$

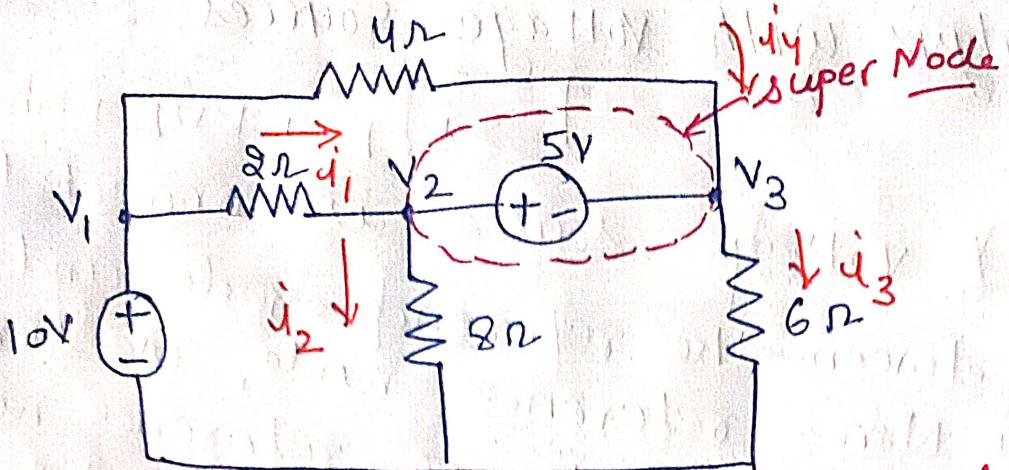

$$i_1 + i_4 = i_2 + i_3$$

$V_2 - V_3$  Node  $\rightarrow$  a super node  
KCL must satisfy at supernode

$$\frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = \frac{V_2 - 0}{8} + \frac{V_3 - 0}{6} \rightarrow ①$$

$$V_2 - V_3 = 5 \rightarrow ②$$


Solve these equation to get node voltages and branch current.

Properties of a Super Node :-

- ① A super node has no voltage of its own.
- ② A super node require the application of KCL & KVL.
- ③ Voltage source inside the super node provides equation needed to solve for node voltages.

(17)

Star to delta conversion

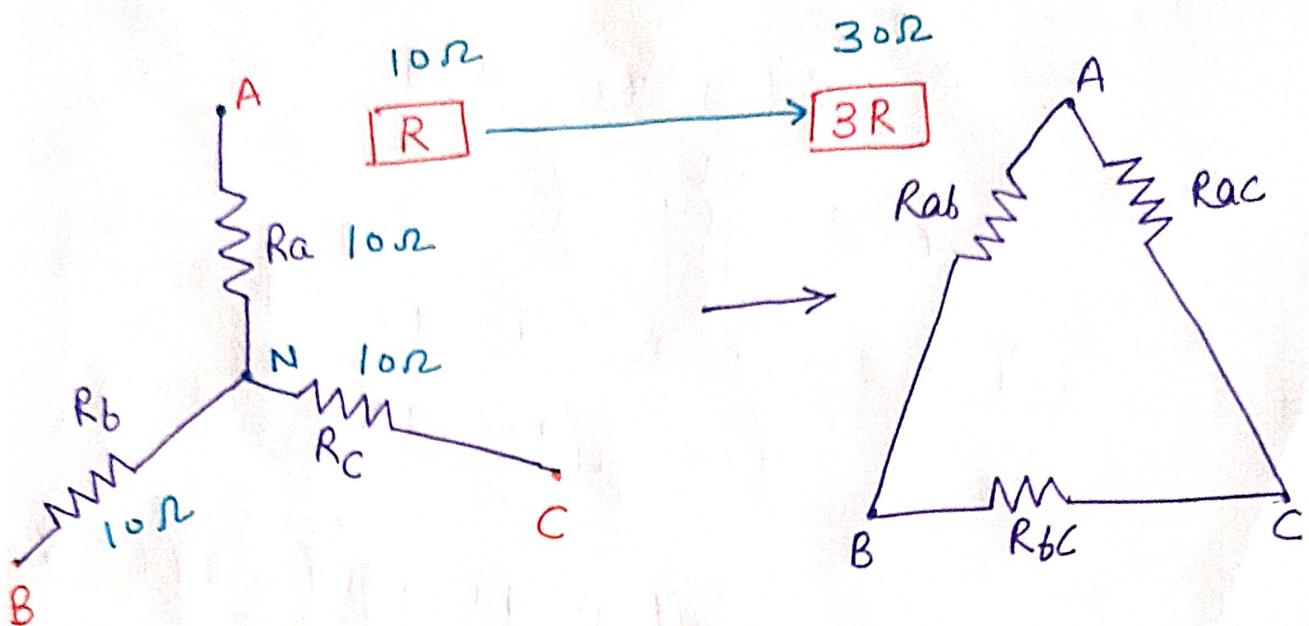

$$R_{AB} = \frac{(10 \times 10) + 10 \times 10 + 10 \times 10}{10} = 30 \Omega$$

$$R_{BC} = R_{AC} = 10 \Omega$$

$$R_A = \frac{R_{AB} \times R_{AC}}{R_{AB} + R_{AC} + R_{BC}} \rightarrow ①$$

$$R_B = \frac{R_{BC} \times R_{AB}}{R_{BC} + R_{AB} + R_{AC}} \rightarrow ②$$

$$R_C = \frac{R_{AB} + R_{BC}}{R_{AB} + R_{AC} + R_{BC}} \rightarrow ③$$

Multiply equation ① & ②

$$R_A \times R_B = \frac{R_{AB}^2 \times R_{AC} \times R_{AC}}{(R_{AB} + R_{BC} + R_{AC})^2} \rightarrow ④$$

$$R_A \times R_C = \frac{R_{AB} \times R_{BC} \times R_{AC}^2}{(R_{AB} + R_{BC} + R_{AC})^2} \rightarrow ⑤$$

$$R_b \times R_c = \frac{R_{ab} \times R_{bc}^2 \times R_{ac}}{(R_{ab} + R_{bc} + R_{ac})^2} \rightarrow ⑥$$

Add ④ - ⑤ - ⑥

$$\begin{aligned} Ra R_b + R_b R_c + R_c Ra &= \frac{R_{ab}^2 R_{bc} R_{ac} + R_{ab} R_{bc}^2 R_{ac} + R_{ab} R_{bc} R_{ca}}{(R_{ab} + R_{bc} + R_{ac})^2} \\ &= \frac{(R_{ab} + R_{bc} + R_{ac})(R_{ab} R_{bc} R_{ca})}{(R_{ab} + R_{bc} + R_{ac})^2} \\ &= \frac{\cancel{R_{ab}} \times \cancel{R_{bc}} \times \cancel{R_{ca}}}{\cancel{R_{ab}} + \cancel{R_{bc}} + \cancel{R_{ca}}} \rightarrow ⑦ \end{aligned}$$



$$Ra R_b + R_b R_c + R_c Ra = R_b \times R_{ca}$$

$$\frac{Ra R_b + R_b R_c + R_c Ra}{R_b} = R_{ca} \quad **$$

$$\frac{Ra R_b + R_b R_c + R_c Ra}{R_c} = R_{ab} \quad **$$

$$\frac{Ra R_b + R_b R_c + R_c Ra}{Ra} = R_{bc} \quad **$$

## Delta - Star Network

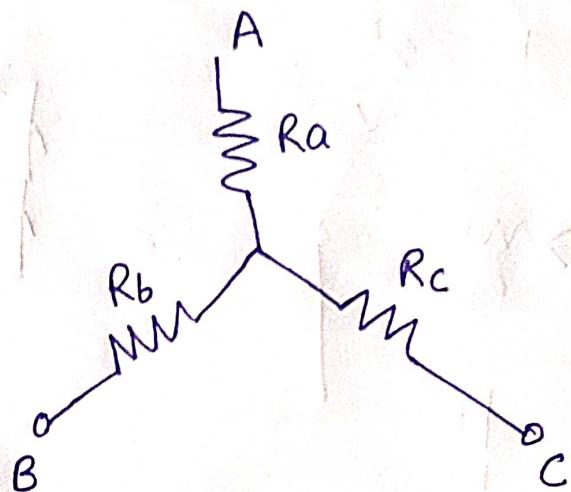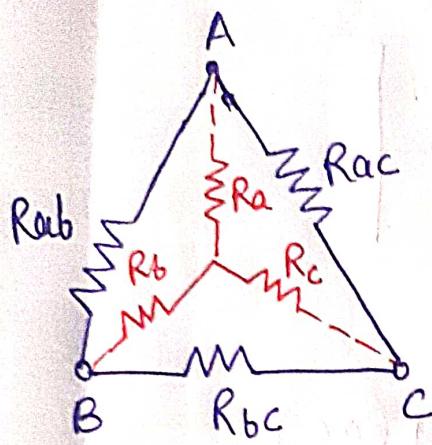


(triangle or  $\Delta$ )

$$Ra = \frac{Rab \times Rac}{Rab + Rbc + Rac} \quad \begin{matrix} \text{Multiplication of adjacent} \\ \text{Resistance} \end{matrix}$$

$$Rb = \frac{Rab \times Rbc}{Rab + Rbc + Rac}$$
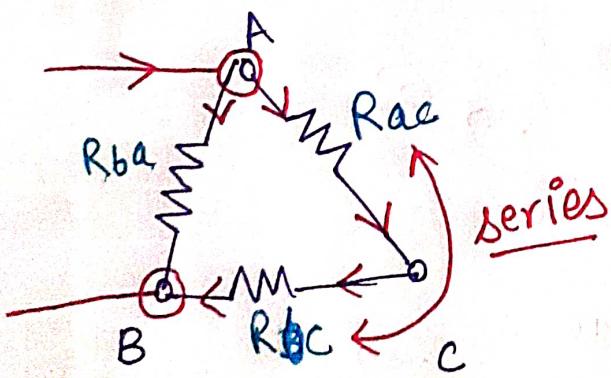
$$Rc = \frac{Rac \times Rbc}{Rab + Rbc + Rac}$$




$Rbc \rightarrow Rac \rightarrow$  series  
Rab in parallel with  
 $Rbc \rightarrow Rac$ .


$$\text{Equation ①} \rightarrow \therefore Ra + Rb = \frac{Rab \times (Rbc + Rac)}{Rab + Rac + Rbc}$$

$$RAB = Rab \parallel (Rac + Rbc)$$
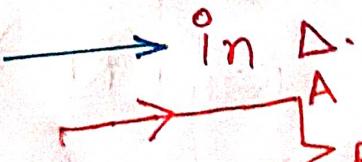
$$RAB = \frac{Rab \times (Rbc + Rac)}{Rab + Rac + Rbc}$$


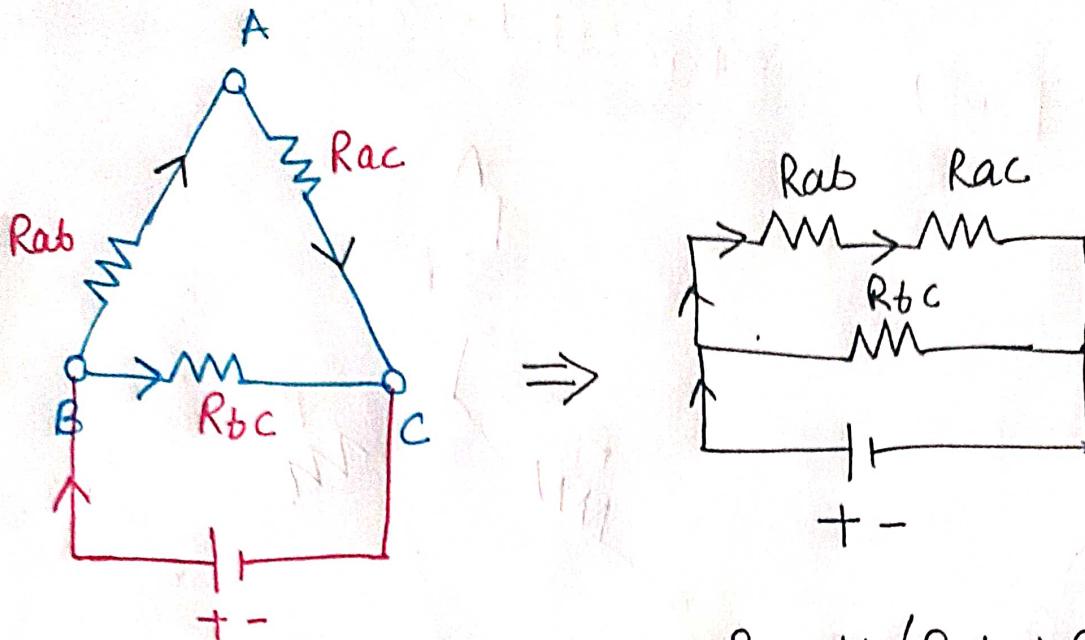
$$Ra + Rb \Rightarrow \frac{Ra + Rb}{Ra + Rb + Rac} = \frac{Rab \times (Rbc + Rac)}{Rab + Rac + Rbc}$$



$R_{ab} + R_{ac}$  (series)

$$\frac{R_{bc} \parallel (R_{ab} + R_{ac})}{R_{bc}}$$

$$\frac{R_{bc} \times (R_{ab} + R_{ac})}{R_{ab} + R_{bc} + R_{ac}}$$

$$= R_b + R_c \rightarrow ②$$

Similarly in Between  $R_a$  &  $R_c$ .

$$\frac{R_{ac} \times (R_{ab} + R_{bc})}{R_{ab} + R_{bc} + R_{ac}}$$

$$= R_a + R_c \rightarrow ③$$

$$R_a + R_b = \frac{(R_{ac} + R_{bc}) R_{ab}}{R_{ab} + R_{bc} + R_{ac}} \rightarrow ①$$

$$R_b + R_c = \frac{(R_{ac} + R_{ab}) \times R_{bc}}{R_{ab} + R_{bc} + R_{ac}} \rightarrow ②$$

$$R_a + R_c = \frac{(R_{ab} + R_{bc}) \times R_{ac}}{R_{ab} + R_{bc} + R_{ac}} \rightarrow ③$$

(3)

(19)

Adding ③ equations

$$2(R_a + R_b + R_c) = \frac{2(R_{ab} * R_{bc} + R_{bc} * R_{ca} + R_{ca} * R_{ab})}{R_{ab} + R_{bc} + R_{ca}}$$


$$R_a + R_b + R_c = \frac{R_{ab} * R_{bc} + R_{bc} * R_{ca} + R_{ca} * R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

For  $R_c$  :-  $R_a + R_b + R_c - R_a + R_b$   
 i.e. eq ④ - ①

$$R_c = \frac{R_{ac} * R_{bc}}{R_{ab} + R_{bc} + R_{ac}}$$

$$R_a = \frac{R_{ab} * R_{ac}}{R_{ab} + R_{bc} + R_{ac}}$$
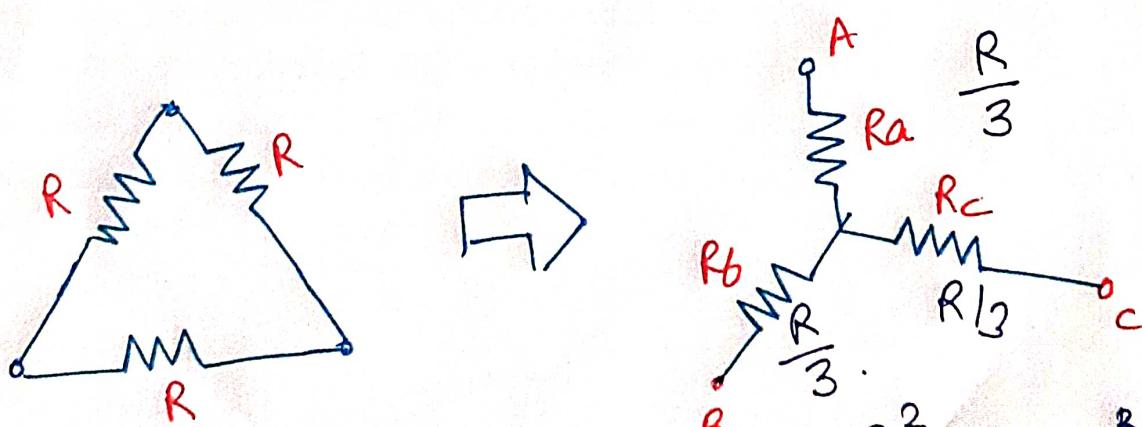
$$R_b = \frac{R_{bc} * R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$



$$R_a = \frac{R * R}{R + R + R} \Rightarrow \frac{R^2}{3R} = \frac{R}{3}$$

# NETWORK THEOREM

DP

Superposition  
Theorem

Thevenin's  
Theorem

Norton's  
Theorem


Maximum  
Power  
Transfer  
Theorem

## ① Thevenin's Theorem

Statement :- A linear active RLC network which contains one or more Independent or dependent voltage and current sources can be replaced by a single voltage source  $V_{oc}$  in series with equivalent Impedance  $Z_{eq}$ .

OR

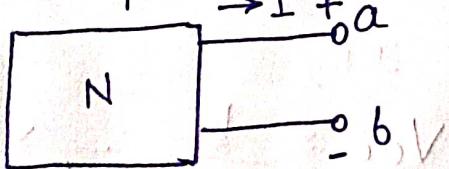It states that a linear two terminal circuit can be replaced by an equivalent circuit consisting of a voltage source  $V_{th}$  in series with  $R_{th}$ . Where  $V_{th}$  is the open circuit voltage at the terminals and  $R_{th}$  is the Input equivalent resistance at the terminals when the independent sources are turned off.




Linear  
Active  
Bilateral  
two  
port N/w

$V_{oc} \rightarrow$  open circuit voltage B/w a & b.  
 $Z_{eq} \rightarrow$  Equivalent Impedance B/w a & b.

When :-

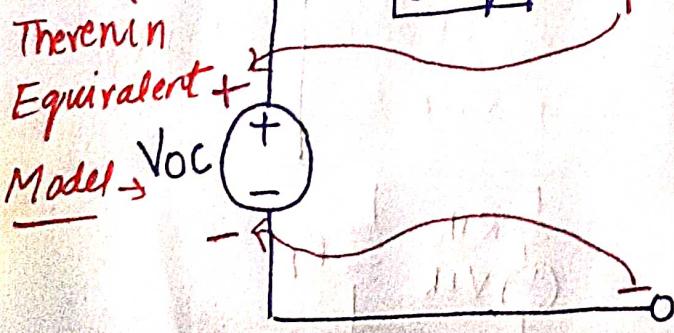- ① All Independent voltage source short circuited.
- ② All independent current source are open circuited.
- ③ All dependent sources remain as they are.



Thevenin  
Equivalent  
Model  $\rightarrow$




Thevenin's equivalent Model

This theorem is not applicable to :-

For the Network contains

- ① Non-linear elements
- ② Unilateral elements

 diode circuits.

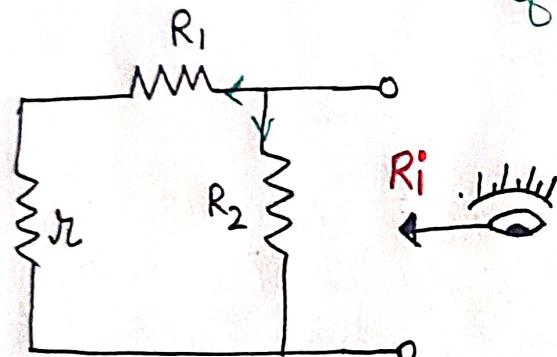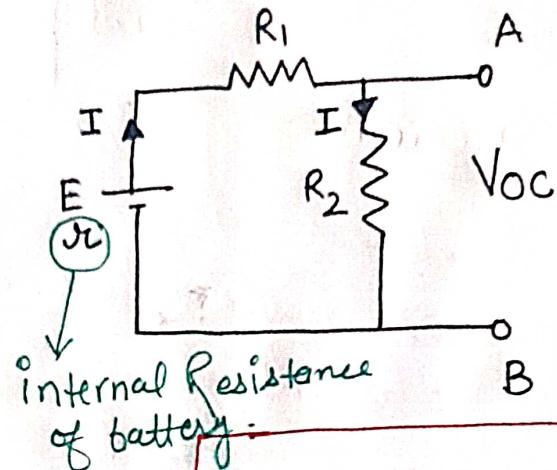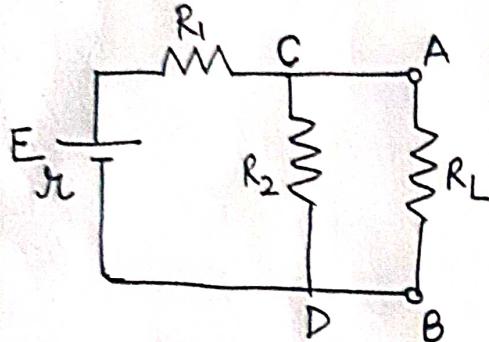

Step ① Suppose we have to find current through  $R_L$ .

Remove  $R_L$  open circuit terminals A & B. Draw the circuit again.

Step ② → Calculate open circuit voltage  $V_{oc}$  which appears across terminals A & B when they are open circuited (i.e.  $R_L$  is removed)

$$V_{oc} \rightarrow \text{drop across } R_2 = IR_2$$

$$I = \frac{E}{R_1 + R_2 + r}$$


$$V_{oc} = \frac{E}{R_1 + R_2 + r} \times R_2$$

Step ③ → Equivalent Resistance  $R = R_2 || (R_1 + r)$

$$*** R = \frac{R_2 (R_1 + r)}{R_2 + R_1 + r} = R_{th.}$$


Step ④ →  $R_L$  Connected Back
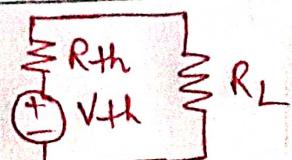
$$\text{Imp} \rightarrow I = \frac{V_{th}}{R_{th} + R_L}$$




## Norton's theorem $\rightarrow$

(21)

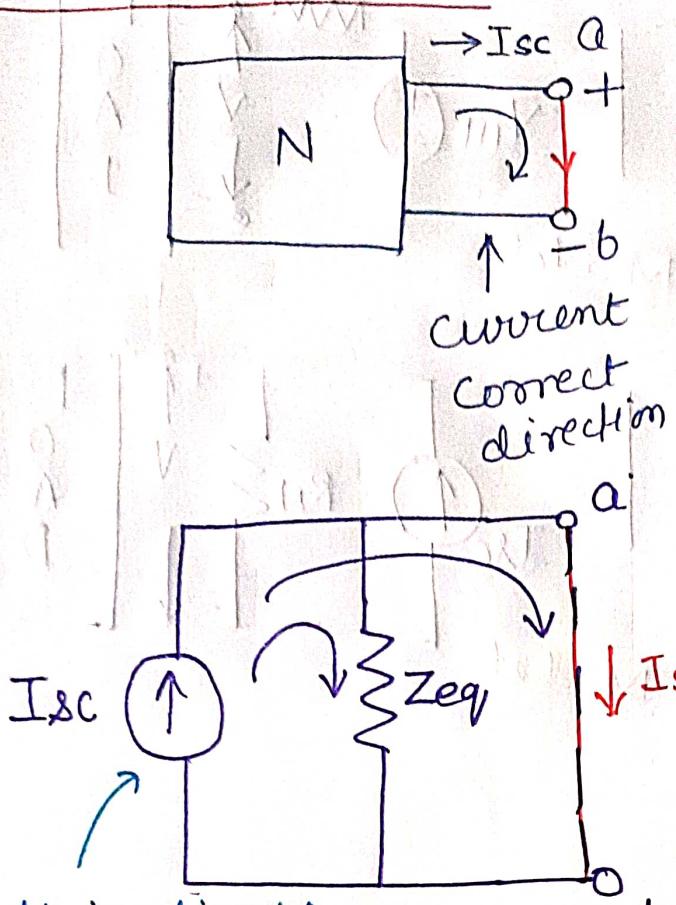

this direction of current indicates current through  $ab$ .

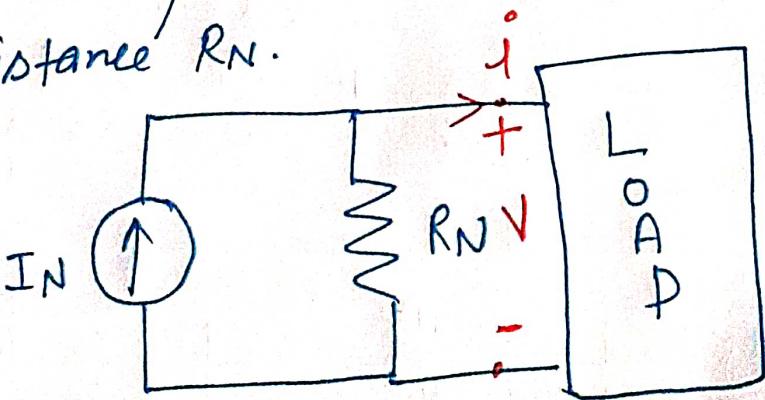Statement: When viewed from load, any network composed of ideal voltage and current sources and of linear resistors, may be represented by an equivalent circuit consisting of an ideal current source  $I_N$  in parallel with an equivalent resistance  $R_N$ .





$I_{sc} \rightarrow$  short circuit current between  $a \& b$ . when  $V=0$

$Z_{eq} \rightarrow$  same as that for Thévenin's Model.



Norton's Model

$$Z_{eq} = \frac{V_{oc}}{I_{sc}}$$

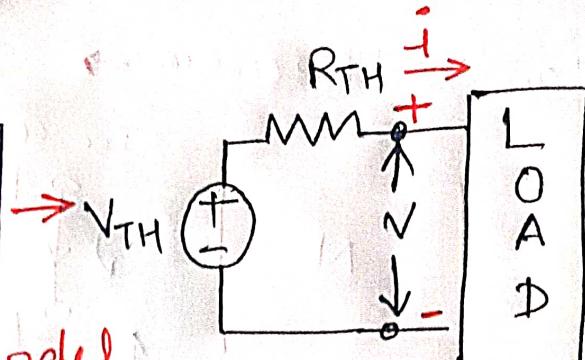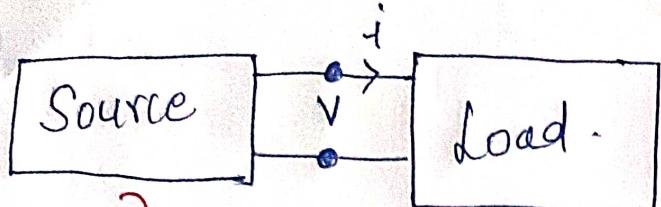

Linear  
Bilateral  
Active  
N.W.

### Thevenin's Model

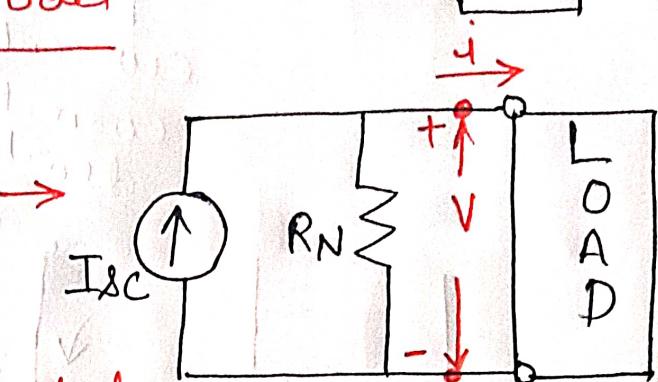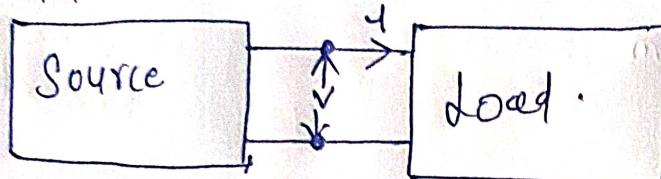


### Norton's Model

## Concept of power absorbed and power delivered


- if current enters into positive terminal of voltage source then it is referred as absorbed power.
- if current leaves positive terminal of voltage source then it is referred as delivered power.

**R, L, C** ← always absorb power

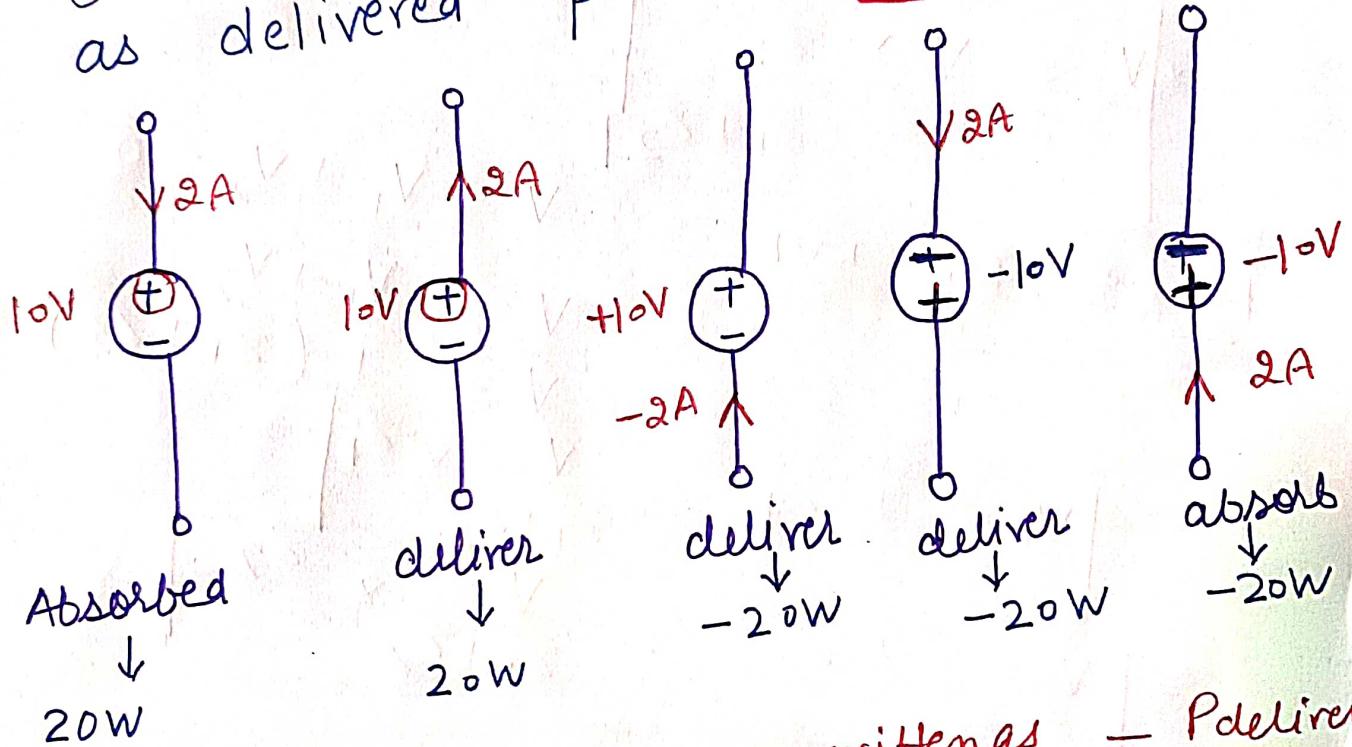

Note's

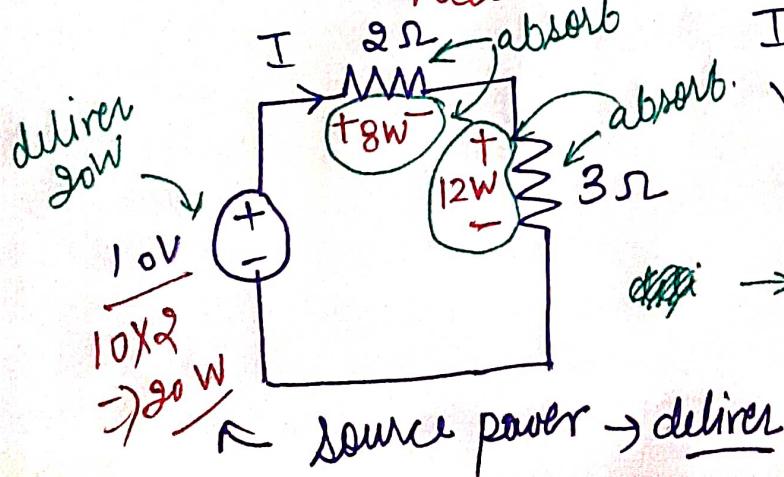$P_{\text{abs}}$  can be written as  $-P_{\text{deliver}}$   
 $P_{\text{deliver}}$  " " " "  
 $P_{\text{abs}}$  " " "




Total Power = Total power delivered  
 Total Power = Total power absorbed

## DIVISION RULE →

- ① Voltage division Rule :-  
 → use in series equivalent circuit for distribution of voltage.

$$* V_1 = V \times \frac{Z_1}{Z_1 + Z_2}$$
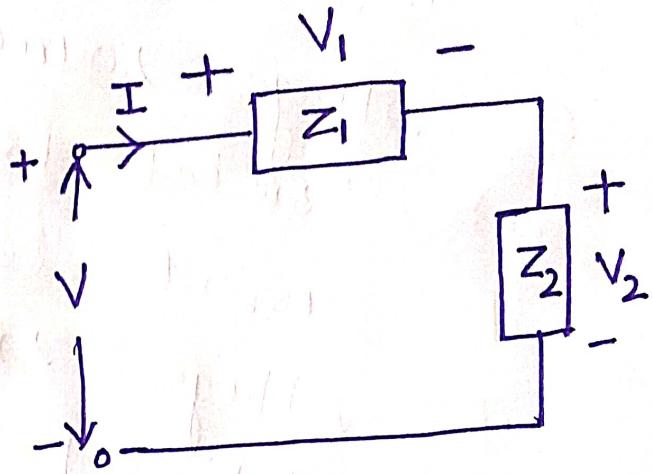
$$* V_2 = V \times \frac{Z_2}{Z_1 + Z_2}$$



Proof :- By KVL :-  $-V + V_1 + V_2 = 0$

$$V = V_1 + V_2$$

$$V = I (Z_1 + Z_2)$$

$$V_1 = I Z_1 = \frac{V}{Z_1 + Z_2} \times Z_1$$


$$V_2 = I Z_2 = \frac{V}{Z_1 + Z_2} \times Z_2$$

### current Division Rule

→ It is used in parallel circuit for distribution of current.

$$\star\star \boxed{I_1 = \frac{I \times Z_2}{Z_1 + Z_2}}$$
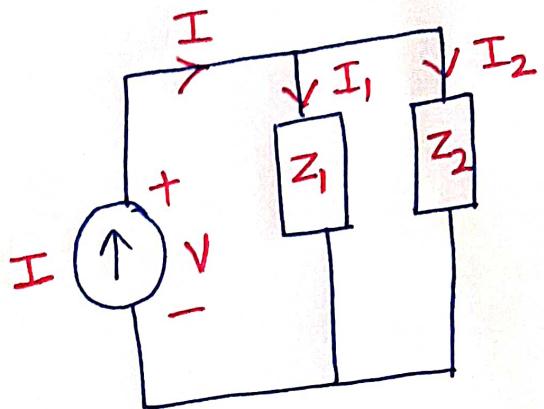
$$\star\star \boxed{I_2 = \frac{I \times Z_1}{Z_1 + Z_2}}$$



Proof :-

$$I = I_1 + I_2$$

$$I = \frac{V}{Z_1} + \frac{V}{Z_2}$$

$$I = V \left[ \frac{Z_1 + Z_2}{Z_1 Z_2} \right]$$

$$\star\star\star \boxed{V = I \times \frac{Z_1 Z_2}{Z_1 + Z_2}}$$

$$\star\star I_1 = \frac{V}{Z_1} = I \times \frac{Z_1 / Z_2}{Z_1 + Z_2} \times \frac{1}{Z_1} = \frac{I \times Z_2}{Z_1 + Z_2}$$

$$\star\star \boxed{I_2 = \frac{V}{Z_2} = I \times \frac{Z_1}{Z_1 + Z_2}}$$